



# Advanced Verilog Design Techniques



# Agenda

- Writing Synthesizable Verilog
- Inferring Common Logic Functions
- Coding State Machines
- Improving Logic Utilization & Performance
- Introduction to Testbenches
- Writing Parameterized Code



# Advanced Verilog Design Techniques

*Writing Synthesizable Verilog*



# Simulation vs. Synthesis

## ■ Simulation

- Code executed in the exact way it is written
- User has flexibility in writing behavioral model
- Initialization of logic supported

## ■ Synthesis

- Code is interpreted & hardware created
  - Knowledge of PLD architecture is important
- Synthesis tools require certain coding to generate correct logic
  - Subset of Verilog language supported
  - Coding style is important for fast & efficient logic
- Initialization controlled by device
  - Logic implementation can be adjusted to support initialization

## ■ Pre- & post-synthesis logic should operate the same



# Writing Synthesizable Verilog

- Synthesizable Verilog constructs
- Sensitivity lists
- Blocking vs. non-blocking
- Latches vs. registers
- **if-else** structures
- **case** statements
- Using functions and tasks
- Combinatorial loops
- Gated clocks

# Some Synthesizable Verilog Constructs

- Module
- Ports
- Parameter
- Net data types
  - wire, tri
  - tri0, tri1
  - wor, wand, trior, triand
  - supply0, supply1
- Variable (register) data types
  - reg, integer
- Assign (continuous)
- Always & initial blocks
- Gates
  - and, nand, nor, or xor, xnor
  - buf, not, bufif0, bufif1, notif0, notif1
- UDPs
- Blocking (=) & non-blocking (<=)
- Sequential blocks (begin/end)
- Tasks & functions
- Bit & part select
- Behavioral constructs
  - If-else statements
  - Case statements
  - Loop statements (with restrictions)
- Disable
- Module instantiation
- Readmemb & readmemh system tasks
- Compiler directives
  - `define, `undef, `ifdef, `else, `endif
  - `include
  - `unconnected\_drive, `nounconnected\_drive
  - `resetall

– *Synthesis tools may place certain restrictions on supported constructs*

– *See the online help in Quartus II (or your target synthesis tool) for a complete list*

– *The Quartus II software supports many constructs not supported by other synthesis tools*

# Some Non-Synthesizable Verilog Constructs

- Net data type
  - trireg
- Variable data types
  - Real, time
- Gates
  - rtran, tran, tranif0, tranif1 rtranif0, rtranif1
- Switches
  - cmos, nmos, rcmos, rnmos, pmos, rpmos
- Pullup & pulldown
- Strengths\*
- Assign (procedural continuous) & deassign
- Force & release
- Delay controls\*
- Event (intra-procedural)
- Named event
- Fork & join
- Specify blocks\*
- `timescale\*
- Most system tasks
  - Display systems tasks\*

*– These are some of the constructs not supported by Quartus II synthesis*  
*– \* = Ignored for synthesis*  
*– See the online help in Quartus II (or your target synthesis tool) for a complete list*

## See:

- [http://eesun.free.fr/DOC/VERILOG/verilog\\_manual1.html#14.1](http://eesun.free.fr/DOC/VERILOG/verilog_manual1.html#14.1)
- <http://www.asic-world.com/verilog/synthesis2.html>
- Quartus II HELP


# Two Types of RTL Processes

- **Combinatorial Process**

- Sensitive to all inputs used in the combinatorial logic

```
always @ (a, b, sel)  
always @ *
```

 *Sensitivity list includes all inputs used  
In the combinatorial logic*




- **Clocked Process**

- Sensitive to a clock or/and control signals

```
always @(posedge clk, negedge clr_n)
```

 *Sensitivity list does not include the d input,  
only the clock and control signals*





# Sensitivity Lists

- Incomplete sensitivity list in an **always** block may result in differences between RTL and gate-level simulations
  - Synthesis assumes complete sensitivity list
  - Should include all inputs to the procedural block (or use @\* shortcut)

```
always @ (a, b)  
  y = a & b & c;
```

**Incorrect Way** – the simulated behavior is not that of the synthesized 3-input AND gate

```
always @ *  
  y = a & b & c;
```

**Correct way for the intended AND logic !**

# Blocking vs. Non-Blocking Recommendations

## ■ Blocking

- Use blocking assignments in combinatorial procedural blocks
- Blocking assignments easier to read
- Blocking assignments uses less memory & simulates faster
  - No scheduling of updated signals

## ■ Non-blocking


- Use non-blocking assignments for clocked procedural blocks

# Clocked Process Example

## Blocking (=)

```
always @(posedge clk)
begin
    a = in;
    b = a;
    out = b;
end
```


### Synthesized Result:

 

## Nonblocking (<=)

```
always @ (posedge clk)
begin
    a <= in;
    b <= a;
    out <= b;
end
```

### Synthesized Result:

 

# Latches vs. Registers

- Altera devices have registers in logic elements, not latches
- Latches are implemented using combinatorial logic & can make timing analysis more complicated
  - Look-up table (LUT) devices use LUTs in combinatorial loops
  - Product-term devices use more product-terms
- Recommendations
  - Design with registers (RTL)
  - Watch out for inferred latches
    - Latches inferred on combinatorial outputs when not results not specified for set of input conditions
    - Lead to simulation/synthesis mismatches

# if-else Structure

- **if-else** structure implies prioritization and dependency

- Nth clause implies all N-1 previous clauses not true
  - Beware of needlessly “ballooning” logic

## Logical Equation

$$(<cond1> \cdot A) + (<\underline{cond1}>' \cdot <cond2> \cdot B) + (<\underline{cond1}>' \cdot <\underline{cond2}>' \cdot <cond3> \cdot C) + \dots$$

- Consider restructuring **if** statements
  - May flatten the multiplexer and reduce logic

IF <cond1> THEN  
    IF <cond2> THEN



IF <cond1> AND <cond2> THEN

- If sequential statements are mutually exclusive, individual **if** structures may be more efficient



# When Writing if-else Structures

- Cover all cases
  - Uncovered cases in combinatorial processes result in latches
- Assign values before reading data type object
  - Reading unassigned data type object results in latches
- For efficiency, consider
  - Using don't cares (X) for final **else** clause (avoiding unnecessary default conditions)
    - Synthesis tool has freedom to encode don't cares for maximum optimization
  - Assigning initial values and explicitly covering only those results different from initial values

# Prioritization & Dependency (if-else)

- Nested **else if** statements imply prioritization and dependency in logic

```
reg [4:0] state;
parameter s0 = 5'h0, s1 = 5'h11, s2 = 5'h12, s3 = 5'h14, s4 = 5'h18;
always @(posedge clk, negedge reset_n) begin
    if (reset_n == 0) state <= s0;
    else begin
        if (state == s0) begin
            if (in == 1) state <= s1; else state <= s0;
        end
        else if (state == s1) state <= s2;
        else if (state == s2) state <= s3;
        else if (state == s3) state <= s4;
        else if (state == s4) begin
            if (in == 1) state <= s1; else state <= s0;
        end
    end
end
end
```

# Prioritization/Dependency Removed (if-else)


- Individual **if** statements where logic is exclusive may be more efficient

```
reg [4:0] state;
parameter s0 = 5'h0, s1 = 5'h11, s2 = 5'h12, s3 = 5'h14, s4 = 5'h18;
always @ (posedge clk, negedge reset_n) begin
    if (reset_n == 0) state <= s0;
    else begin
        if (state == s0) begin
            if (in == 1) state <= s1; else state <= s0;
        end
        if (state == s1) state <= s2;
        if (state == s2) state <= s3;
        if (state == s3) state <= s4;
        if (state == s4) begin
            if (in == 1) state <= s1; else state <= s0;
        end
    end
end
```
 
# Unwanted Latches

- Combinatorial processes that do not cover all possible input conditions generate latches

```
always @ *  
begin  
    if (sel == 3'b001)  
        out = a;  
    else if (sel == 3'b010)  
        out = b;  
    else if (sel == 3'b100)  
        out = c;  
end
```




# Unwanted Latches Removed
 
## ■ Close all **if-else** structures

- If possible, assign “don’t care’s” to else clause for improved logic optimization

```
always @ *  
begin  
    if (sel == 3'b001)  
        output = a;  
    else if (sel == 3'b010)  
        output = b;  
    else if (sel == 3'b100)  
        output = c;  
    else  
        output = 3'bx;  
end
```





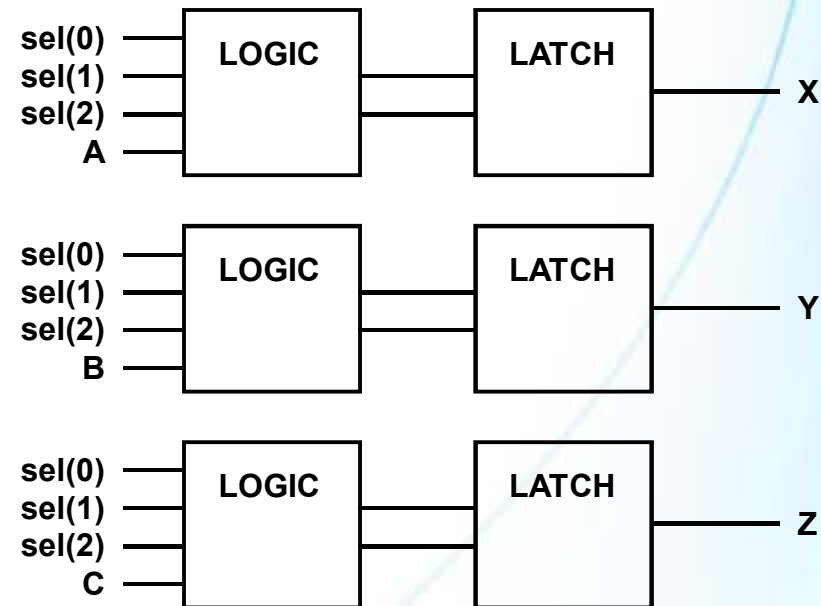
# Mutually Exclusive if-else Latches

- Beware of building unnecessary dependencies
  - e.g. Outputs x, y, z are mutually exclusive, **if-else** causes all outputs to be dependant on all tests & creates latches


```
always @ (sel,a,b,c)
begin
    if (sel == 3'b010)
        x = a;
    else if (sel == 3'b100)
        y = b;
    else if (sel == 3'b001)
        z = c;
    else
        x = 0;
        y = 0;
        z = 0;
end
```


 
# Mutually Exclusive Latches Removed

- Use separate **if** statements and close each with initialization or **else** clause

```
always @ (sel,a,b,c)
begin
    x = 0;
    y = 0;
    z = 0;
    if (sel == 3'b010)
        x = a;
    if (sel == 3'b100)
        y = b;
    if (sel == 3'b001)
        z = c;
end
```




# Unwanted Latches – Nested if Statements

- Use nested **if** statements with care
  - e.g. These nested **if** statements do not cover all possible conditions (open **if** statements) & latch is created

```
always @ (ina, inb)
begin
    if (ina == 1) begin
        if (inb == 1) out = 1;
        end
    else out = 0;
end
```

<u>ina</u>	<u>inb</u>	<u>out</u>
1	1	1
0	0	0
0	1	0
1	0	?

 


- Uncovered cases infer latches
  - No default value for data type objects
- Equation
  - $A1L3 = LCELL(ina \& (A1L3 \# inb));$

# Unwanted Latches Removed – Nested if Statements

```
always @ (ina, inb)
begin
    out = 0;
    if (ina == 1)
        if (inb == 1)
            out = 1;
end
```

<u>ina</u>	<u>inb</u>	<u>out</u>
1	1	1
0	0	0
0	1	0
1	0	0

 


- Using initialization to cover all cases; no latch inferred
- Equation
  - $A1L3 = inb \ \& \ ina;$
 
# Variable Not Initialized

- Reading a variable data type object in a combinatorial process before it has been assigned a value infers a latch

```
always @ *  
begin  
    if (a == 1) val = val;  
    else val = val + 1'b1;  
    case (val)  
        1'b0 : q = i[0];  
        1'b1 : q = i[1];  
    endcase  
end
```





 
# Assigning Initial Value to Variable

- Assigning a value to a data type object prior to reading it prevents a latch

```
always @ *  
begin  
    val = 1'b0;  
    if (a == 1) val = val;  
    else val = val + 1'b1;  
    case (val)  
        1'b0 : q = i[0];  
        1'b1 : q = i[1];  
    endcase  
end
```



# Case Statements

- Case statements usually synthesize more efficiently when mutual exclusivity exists
- When writing case statements
  - Make sure all case items are unique/parallel
    - Verilog language does not require this
    - Non-parallel cases infer priority encoders (i.e. less efficient logic)
  - Cover all cases
    - Like **if-else**, uncovered cases infer latches
    - Caused by
      - Incomplete case statement
      - Outputs not defined for one case item

# Case Statement Recommendations

- Initialize all case outputs or ensure outputs assigned in each case
- Use **default** clause to close undefined cases (if any remain)
- Assign initialized or default values to don't cares (X) for further optimization, if logic allows

# Case Statement Example

```
always @ *  
begin  
  // in1 = 32'bx;  
  case (state)  
    4'b0000: in1 = data_a;  
    4'b1001: in1 = data_b;  
    4'b1010: in1 = data_c;  
    4'b1100: in1 = data_d;  
  endcase  
end
```

*Incomplete case*



```
always @ *  
begin  
  case (state)  
    4'b0000: in1 = data_a;  
    4'b1001: in1 = data_b;  
    4'b1010: in1 = data_c;  
    4'b1100: in1 = data_d;  
    default: in1 = 32'bx;  
  endcase  
end
```

*Completed case*

# “Full” Case

- Definition: All possible case-expression binary patterns can be matched to a case item or a case default
- Non-full case statements infer latches
- Adding “full\_case” synthesis directive to non-full case statements
  - Used to reduce logic count as synthesis accounts only for defined possibilities
  - May cause pre-synthesis and post-synthesis simulation mismatch

## Mismatched Code (BAD)

```
always @ (ena or a) begin
    case ({ena,a}) //synthesis full_case
        2'b1_0: out[a] = 1'b1;
        2'b1_1: out[a] = 1'b1;
    endcase
end
```

## Full Statement (GOOD)

```
always @ (ena or a) begin
    case ({ena,a})
        2'b1_0: out[a] = 1'b1;
        2'b1_1: out[a] = 1'b1;
        default: out = 2'bxx;
    endcase
end
```



# “Parallel” Case

- Definition: Only possible to match a case expression to one and only one case item
- Non-parallel case statements infer priority encoders
  - Code all intentional priority encoders with if-else statements for clarity
- Adding “parallel\_case” synthesis directive to non-parallel case statement
  - Used to reduce the logic size as synthesis tool removes priority
  - May cause pre-synthesis and post-synthesis simulation mismatch

## Mismatched Code (BAD)

```
always @ (a) begin
    casez (a) //synthesis parallel_case
        3'b1??: out = 2'b01;
        3'b?1?: out = 2'b10;
        3'b??1: out = 2'b11;
    endcase
end
```

## Non-Prioritized Code (GOOD)

```
always @ (a) begin
    case (a)
        3'b100: out = 2'b01;
        3'b010: out = 2'b10;
        3'b001: out = 2'b11;
        default: out = 2'bxx;
    endcase
end
```


# Using Functions & Tasks

- Functions and tasks can be used in synthesized modules to make code more readable/reusable
- Functions
  - Synthesize to combinational logic
  - Variables in functions must be local
- Tasks
  - Synthesize to combinational or sequential logic
  - Cannot contain time delay
- Each call generates a separate block of logic
  - No logic sharing
  - Implement resource sharing, if possible (discussed later)
 
# Combinational Loops

- Common cause of instability
- Behavior of loop depends on the relative propagation delays through logic
  - Propagation delays can change
- Simulation tools may not match hardware behavior

```
always @ (posedge clk, negedge clrn)
begin
    if (!clrn)
        q <= 0;
    else
        q <= d;
end
assign clrn = (ctrl1 ^ ctrl2) & q;
```




# Combinational Loops

- All feedback loops should include registers

```
always @ (posedge clk, negedge clrn)
begin
    if (!clrn)
        q <= 0;
    else
        q <= d;
end

 always @ (posedge clk)
    clrn <= (ctrl1 ^ ctrl2) & q;
```



# Gated Clocks

- Can lead to both functional and timing problems
  - Clock behavior subject to both synthesis and placement & routing
  - Can be a source of additional clock skew
  - Glitches on clock path possible
- Recommendations:
  - Use clock enables for clock gating functionality
  - Use dedicated device resources (e.g. clock control blocks) to gate clocks synchronously and reduce power
  - If you must build your own gating logic
    - Use a synchronous gating structure
    - Ensure global clock routing is used for clock signal
    - Gate the clock at the source

# Gated Clock Examples

```
assign g_clk = gate & clk;
```

```
always @ (posedge g_clk, negedge clrn)
begin
    if (!clrn)
        q <= 0;
    else
        q <= d;
end
```

Poor clock gating – Active clock edges occurring near gate signal changes may result in glitches

```
always @ (negedge clk)
    sgate = gate
```

```
assign g_clk = sgate & clk;
```

```
always @ (posedge g_clk, negedge clrn)
begin
    if (!clrn)
        q <= 0;
    else
        q <= d;
end
```

Better clock gating – Gate signal clocked by falling edge clk, so gate may only change on inactive clock edge (Use OR gate when falling edge is the active clock edge)





# Advanced Verilog Design Techniques

*Inferring Common Logic Functions*





# Inferring Logic Functions


- Using behavioral modeling to describe logic blocks
- Synthesis tools recognize description & insert equivalent logic functions (e.g. megafunctions)
  - Functions typically pre-optimized for utilization or performance over general purpose functionally equivalent logic
  - Use synthesis tool's templates (if available) as starting point
  - Use synthesis tool's graphic display to verify logic recognition
- Makes code vendor-independent

# Logic Inference Example

```
always @ (posedge clock)
begin
    if (wren)
        mem[address] <= data;
    q <= mem[address_out];
end
```

*Synthesis tool sees*

*Replaces with*

 

*Altera megafunction and/or library cells*

# Verilog Templates

The screenshot shows the Quartus II software interface. The main window displays a Verilog HDL file with a list of templates on the left. The 'Insert Template' dialog box is open, showing a tree view of templates. The 'Binary Up/Down Counter' template is selected. The 'Preview' window shows the Verilog code for the selected template. A yellow callout box points to the 'Insert Template' button in the main window. Another yellow callout box points to the 'Preview' window, stating: 'Preview window: edit before inserting & save as user template'. A third yellow callout box points to the 'Save User Template' dialog box, which is open and shows the 'User template name' field with the text 'my\_binary\_counter'.

**Insert Template (Edit menu)**

**Preview window: edit before inserting & save as user template**

**Save User Template**

User template name:

OK Cancel

Save Insert Close

© 2009 Altera Corporation—**Confidential**


ALTERA, ARRIA, CYCLONE, HARDCOPY, MAX, MEGACORE, NIOS, QUARTUS & STRATIX are Reg. U.S. Pat. & Tm. Off. and Altera marks in and outside the U.S.

# Inferring Common Functions

- Latches
- Registers
- Counters
- Tri-states
- Memory
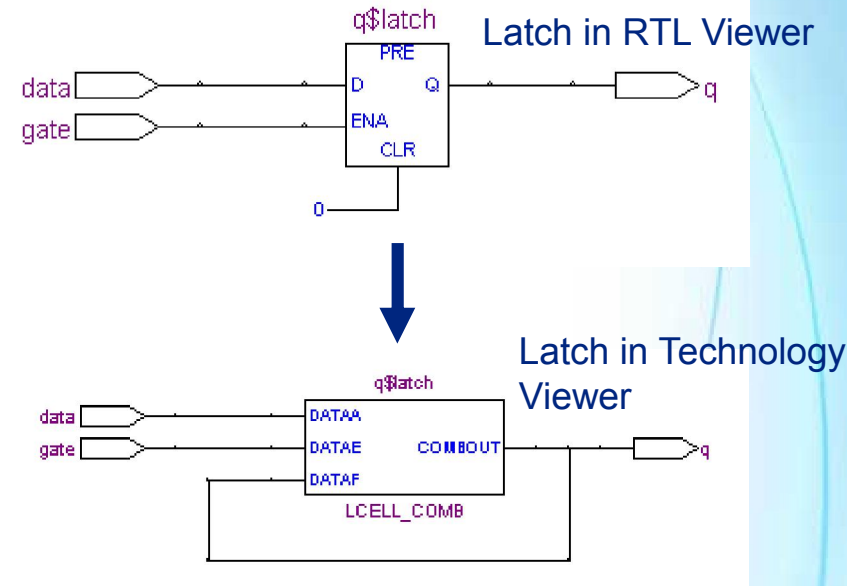
# “Wanted” Latches

```
module latches (  
    input d, gate;  
    output reg q  
);  
  
wire d, gate;  
  
always @(d, gate)  
  
    if (gate)  
        q = d;  
endmodule
```



*sensitivity list includes both inputs*


*level sensitive...not edge*

*What happens if gate = '0'?*

⇒ **Implicit Memory & Feedback**
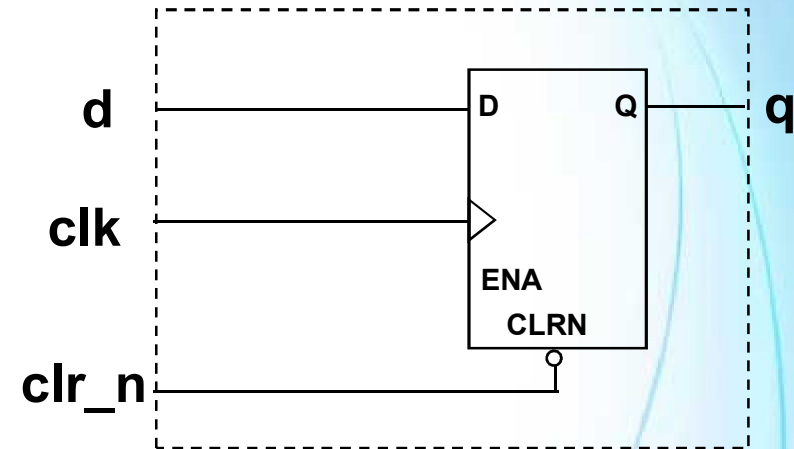
# Inferring Flip-Flops

```
module basic_dff (  
    input clk, d, clr_n;  
    output reg q;  
);  
always @(posedge clk, negedge clr_n)  
    if (!clr_n)  
        q <= 0;  
    else  
        q <= d;  
endmodule
```



- Simple register logic with reset
- Recommendation: Always use reset (asynchronous or synchronous) to get system into known or initial state

# Secondary Control Signals

- Register control signals vary between FPGA & CPLD families
  - Clear, preset, load, clock enable, etc.
- Avoid using signals not available in architecture
  - Functionality of design supported by creating extra logic cells
  - Less efficient, possibly slower results



# DFF with Secondary Control Signals


```
module dff_full (  
    input clk, ena, d,  
    input clr_n, sclr, pre_n,  
    input aload, sload, adata, sdata,  
    output reg q  
);  
  
always @(posedge clk, negedge clr_n,  
        negedge pre_n, posedge aload)  
    if (!clr_n)  
        q <= 1'b0;  
    else if (!pre_n)  
        q <= 1'b1;  
    else if (aload)  
        q <= adata;  
    else if (ena)  
        if (sclr)  
            q <= 1'b0;  
        else if (sload)  
            q <= sdata;  
        else  
            q <= d;  
endmodule
```

- *This is how to implement all asynchronous and synchronous control signals for the Altera PLD registers*
  - *Conditions in the sensitivity list are asynchronous*
  - *Conditions not in the sensitivity list are synchronous*
- *Remove signals not required by your logic*
  - *Most PLD architectures would require additional logic to support all at once*
- *Why is this asynchronous signal **adata** left out of the sensitivity list?*
  - *Verilog limitation*
  - *Inferred correctly (simulation mismatch)*
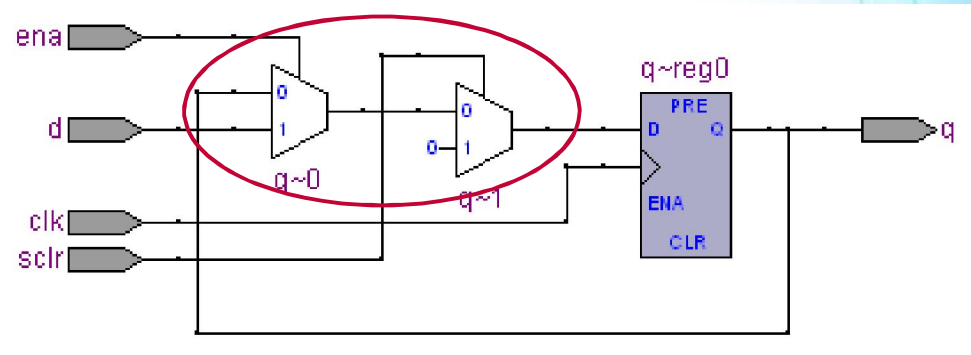
# Incorrect Control Signal Priority

```
module dff_sclr_ena (
    input clk, d, ena, sclr,
    output reg q
);

always @ (posedge clk)
    if (sclr)
        q <= 1'b0;
    else if (ena)
        q <= d;
endmodule
```



- 2 control signals
- Considerations
  - Do the registers in the hardware have both ports available?
  - How does hardware behave? Does clear or enable have priority?
- Sync clear has priority enable over in code
- Enable has priority over sync clear in silicon
- Additional logic needed to force code priority


# Control Signal Priority

1. Asynchronous clear (aclr)
  2. Asynchronous preset (pre)
  3. Asynchronous load (aload)
  4. Enable (ena)
  5. Synchronous clear (sclr)
  6. Synchronous load (sload)
- Same for all Altera FPGA families
    - All signals not supported by all families
  - Re-ordering may generate extra logic
 
# Incorrect Control Logic


```
module dff_inc (  
    input clk, reset_n, a, b,  
    output reg x, y  
);  
always @(posedge clk, negedge reset_n)  
    if (reset_n == 0)  
        x <= 0;  
    else begin  
        x <= a;  
        y <= b;  
    end  
endmodule
```

- ***y*** Is Not Included in Reset Condition
- ***reset*** Clears ***x*** but Acts More Like an Enable for ***y***



# DFF with Clock Enable

```
module dff_ena (  
    input clk, clr_n, d,  
    input ena_a, ena_b, ena_c,  
    output reg q  
);  
  
    always @ (posedge clk, negedge clr_n)  
        if (clr_n == 1'b0)  
            q <= 1'b0;  
        else if (ena == 1'b1)  
            q <= d;  
  
    assign ena <=  
        (ena_a | ena_b) ^ ena_c;  
  
endmodule
```

 


- To ensure that this is synthesised using DFFE primitives (DFF with enable)
  - Place the enable statement directly after the rising edge statement
  - Place enable expressions in separate process or assignment
- If the synthesis tool does not recognize this as an enable it will be implemented using extra LUTs
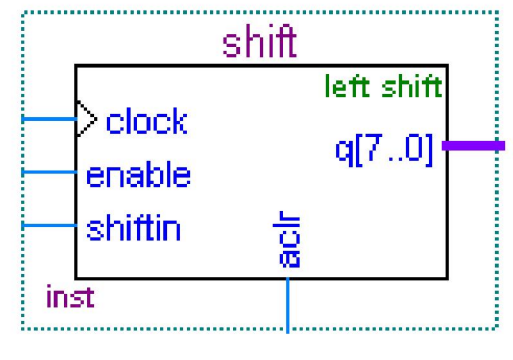
# Shift Registers

```
module shift (  
    input aclr_n, enable, shiftin, clock,  
    output reg [7:0] q  
);  
always @(posedge clock, negedge aclr_n)  
    if (!aclr_n)  
        q[7:0] <= 0;  
    else if (enable)  
        q[7:0] <= {q[6:0], shiftin};  
endmodule
```

- Shift register with parallel output, serial input, asynchronous clear and enable which shifts left
- Add or remove synchronous controls in a manner similar to DFF




*Shift function*

- Use { , } for concatenation
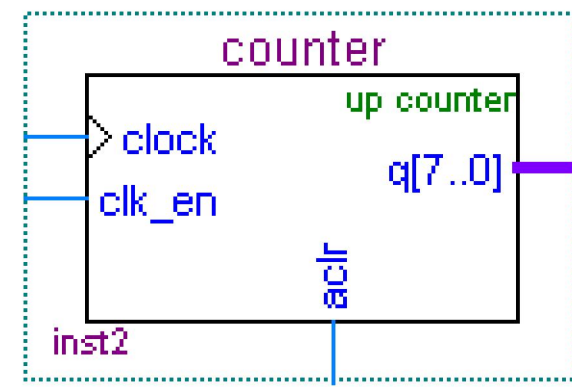
# Basic Counter w/Async Clear & Clock Enable

```
module count (  
    input clk, aclr_n, ena,  
    output reg [7:0] q = 0  
);  
  
always @(posedge clk, negedge aclr_n)  
    if (!aclr_n)  
        q[7:0] <= 0;  
    else if (ena)  
        q <= q + 1;  
  
endmodule
```




Count function

- Binary up counter with asynchronous clear and clock enable
- Add or remove secondary controls similar to DFF


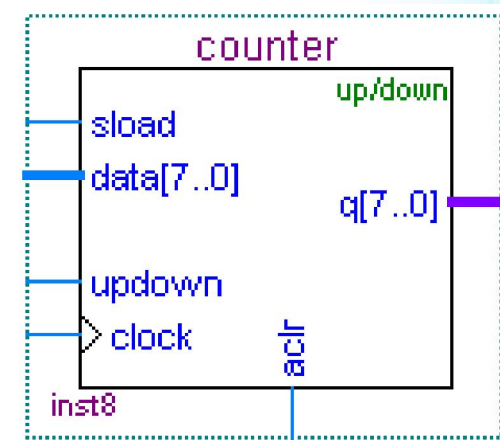
# Up/Down Counter w/Sync Load

```
module count (  
    input clk, aclr_n, updown, sload,  
    input [7:0] data,  
    output reg [7:0] q = 0  
);  
always @ (posedge clk, negedge aclr_n)  
begin  
    if (aclr_n == 0)  
        q[7:0] <= 0;  
    else if (sload == 1)  
        q <= data;  
    else begin  
        q <= q + (updown ? 1 : -1);  
    end  
end  
endmodule
```




*Up/down behavioral description*
 
# Modulus-100 Up Counter

```
module count
    #(parameter modulus = 100)
    (
        input clk, aclr_n,
        output reg [7:0] q = 0
    );

    always @(posedge clk, negedge aclr_n)
    begin
        if (aclr_n == 0)
            q[7:0] <= 0;
        else begin
            if (q == modulus - 1)
                q <= 8'd0;
            else
                q = q + 1;
        end
    end
end
endmodule
```




# Tri-States

- IEEE-defined 'Z' or 'z' value
  - Simulation: Behaves like high-impedance state
  - Synthesis: Converted to tri-state buffers
- Altera devices have tri-state buffers only in I/O cells
  - Benefits:
    - Eliminates possible bus contention
    - Location of internal logic is a non-issue
    - Cost savings
      - Don't pay for unused tri-state buffers
      - Less testing required of devices
  - Internal tri-states must be converted to combinatorial logic
  - Complex output enable may cause errors or inefficient logic
- The **wire** and **tri** keywords have identical syntax and function
  - Use **wire** to indicate a net with a single driver
  - Use **tri** to indicate a net that can have multiple drivers

# Inferring Tri-States Correctly
 
## Conditional Signal Assignment


```
module dff_1(in_sig, ena, out_sig);  
  
  input in_sig, ena;  
  output tri out_sig;  
  
  assign out_sig = ena ? in_sig : 1'bZ;  
  
endmodule
```



- Only 1 Assignment to Output Variable
- Uses Tri-State Buffer in I/O Cell
  - **out\_sig** should connect directly to top-level I/O pin (through hierarchy is ok)
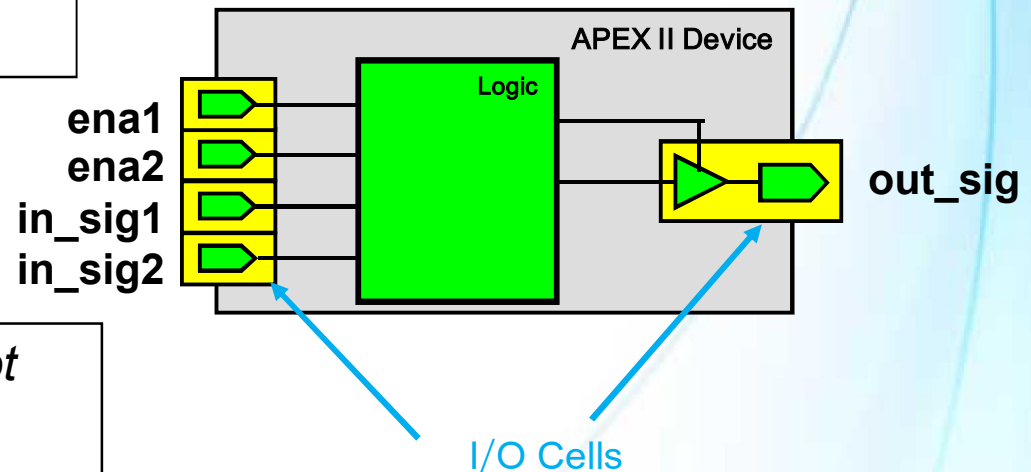
# Inferring Tri-states Incorrectly

```
module dff_1(in_sig, ena, out_sig);  
  
  input in_sig, ena;  
  output tri out_sig;  
  
  assign out_sig = ena1 ? in_sig1 : 1'bZ;  
  assign out_sig = ena2 ? in_sig2 : 1'bZ;  
  
endmodule
```



- 2 Assignments to Same Signal Not Allowed in Synthesis Unless 'Z' Is Used
- Output Enable Logic Emulated in LEs
- Simulation & Synthesis Do Not Match

© 2009 Altera Corporation—**Confidential**

ALTERA, ARRIA, CYCLONE, HARDCOPY, MAX, MEGACORE, NIOS, QUARTUS & STRATIX are Reg. U.S. Pat. & Tm. Off. and Altera marks in and outside the U.S.

# Bidirectional Pins

```
module module_name (  
    ...,  
    inout bidi,  
    ...  
);  
  
wire incoming_signal;  
  
assign incoming_signal = bidi;  
  
logic operating on incoming_signal  
logic generating outgoing_signal  
  
assign bidi = (oe ? outgoing_signal : 1'bZ);
```

- Declare Pin As Direction ***inout***
- Use ***inout*** As Both Input & Tri-State Output
- For registered bidirectional I/O, use separate process to infer registers

*bidi as an input*

*bidi as an tri-stated output*

# Memory

- Synthesis tools have different capabilities for recognizing memories
- Synthesis tools are sensitive to certain coding styles in order to recognize memories
  - Usually described in the tool documentation (e.g. Quartus II Handbook)
- Tools may have limitations in architecture implementation
  - Newer Altera devices support synchronous inputs only
  - Limitations in clocking schemes
  - Memory size limitations
  - Read-during-write support
- Must create an array variable to hold memory values



# Inferred Single-Port Memory (1)

```
module sp_ram_async_read (  
    output [7:0] q,  
    input [7:0] d,  
    input [6:0] addr,  
    input we, clk  
);
```

```
reg [7:0] mem [127:0];
```

```
always @(posedge clk)  
    if (we)  
        mem[addr] <= d;
```

```
assign q = mem[addr];
```

```
endmodule
```

Memory array

- Code describes a **128 x 8 RAM** with synchronous write & asynchronous read
- **Cannot be implemented in Altera embedded RAM due to asynchronous read**
  - Uses general logic and registers

# Inferred Single-Port Memory (2)

```
module sp_ram_sync_rdwo (  
    output reg [7:0] q,  
    input [7:0] d,  
    input [6:0] addr,  
    input we, clk  
);
```

```
reg [7:0] mem [0:127];
```

```
always @(posedge clk)  
begin
```

```
    if (we)  
        mem[addr] <= d;  
    q <= mem[addr];
```

```
end
```

```
endmodule
```



- Code describes a **128 x 8 RAM** with synchronous write & synchronous read
- Old data read-during-write behaviour
  - Memory read in same process/cycle as memory write using **non-blocking** statements
  - Check target architecture for support as unsupported features built using LUTs/registers

**Recommendation:** Read Quartus II Handbook, Volume 1, Chapter 6 for more information on inferring memories and read during write behavior

# Inferred Simple Dual-Port Memory

```
module sdp_sc_ram (  
    output reg [7:0] q,  
    input [7:0] d,  
    input [6:0] wr_addr, rd_addr,  
    input we, clk  
);  
  
reg [7:0] mem [0:127];  
  
always @(posedge clk) begin  
    if (we)  
        mem[wr_addr] <= d;  
    q <= mem[rd_addr];  
end  
  
endmodule
```

- Code describes a **simple dual-port** (separate read & write addresses) 64 x 8 RAM with single clock
- Code implies old data read-during-write behaviour
  - New data support in simple dual-port requires additional RAM bypass logic

# Inferred Dual-Port Memory

```
module dp_dc_ram (  
    output reg [7:0] q_a, q_b,  
    input [7:0] data_a, data_b,  
    input [6:0] addr_a, addr_b,  
    input clk_a, clk_b, we_a, we_b  
);
```

```
reg [7:0] mem [0:127];
```

```
always @(posedge clk_a)  
begin  
    if (we_a)  
        mem[addr_a] <= data_a;  
    q_a <= mem[addr_a];  
end
```

```
always @(posedge clk_b)  
begin  
    if (we_b)  
        mem[addr_b] <= data_b;  
    q_b <= mem[addr_b];  
end  
endmodule
```

- Code describes a **true dual-port** (two individual addresses) 64 x 8 RAM with dual clocks
- May not be supported in all synthesis tools
- Old data same-port read-during-write behaviour shown
  - Supported only in Stratix III, Stratix IV and Cyclone III devices
  - Other device families support new data (blocking assignments)
- Mixed port behaviour undefined with multiple clocks

# Initializing Memory Contents

```
module ram_init (  
    output reg [7:0] q,  
    input [7:0] d,  
    input [6:0] wr_addr, rd_addr,  
    input we, clk  
);  
reg [7:0] mem [0:127];  
  
initial  
    $readmemh("ram.dat", mem);  
  
always @(posedge clk) begin  
    if (we)  
        mem[wr_addr] <= d;  
    q <= mem[rd_addr];  
end  
  
endmodule
```

- Use *\$readmemb* or *\$readmemh* system tasks to assign initial contents to inferred memory
- Initialization data stored in .dat file converted to **.MIF** (Altera memory initialization file)
- Contents of .MIF downloaded into FPGA during configuration
- Alternate: Use an initial block and loop to assign values to array address locations

# Using System Tasks to Initialize Memory

- Each number in file given separate address
  - White spaces and comments separate numbers
- Examples
  - \$readmemb (“<file\_name>”, <memory\_name>);
  - \$readmemb (“<file\_name>”, <memory\_name>, <mem\_start\_addr>);
  - \$readmemb (“<file\_name>”, <memory\_name>, <mem\_start\_addr>, <mem\_finish\_addr>);
- <mem\_start\_addr> and <mem\_finish\_addr> are optional
  - Indicate beginning and ending memory addresses in which data will be loaded
    - Addresses can be ascending or descending
  - Defaults are the start index of the memory array and the end of the data file or memory array
  - Uninitialized addresses will be don't care's (X's) for synthesis and will be loaded with 0's by Quartus II software

*ram.dat*

```
0000_0000
0000_0101
0000_1010
0000_1111
0001_0100
0001_1001
0001_1110
0010_0011
0010_1000
// Repeat segment at
// address 20 hex
@20
0000_0000
0000_0101
0000_1010
0000_1111
0001_0100
0001_1001
0001_1110
0010_0011
0010_1000
```



# Unsupported Control Signals

## ■ e.g. Clearing RAM contents with reset

```
module ram_unsupported (  
    output reg [7:0] q,  
    input [7:0] d,  
    input [6:0] addr,  
    input we, clk  
);  
reg [7:0] mem [0:127];  
  
always @(posedge clk, negedge aclr_n)  
begin  
    if (!aclr_n) begin  
        mem[addr] <= 0;  
        q <= 0;  
    end  
    else if (we) begin  
        mem[addr] <= d;  
        q <= mem[addr];  
    end  
end  
  
endmodule
```

- *Memory content cannot be cleared with reset*
- *Synthesizes to logic*
- *Recommendations*
  1. *Avoid reset checking in RAM read or write processes*
  2. *Be wary of other control signals (i.e. clock enable) until validated with target architecture*



# Inferred ROM (Case)

```
reg [6:0] q;  
  
always @ (posedge clk)  
begin  
    case (addr)  
        6'b000000: q <= 8'b01111111;  
        6'b000001: q <= 8'b00111000;  
        6'b000010: q <= 8'b11011101;  
        6'b000011: q <= 8'b11111100;  
        6'b000100: q <= 8'b10111010;  
        6'b000101: q <= 8'b11101110;  
        ...  
        6'b111101: q <= 8'b11101111;  
        6'b111110: q <= 8'b00111100;  
        6'b111111: q <= 8'b11111111;  
    end case  
end
```

- *Automatically converted to ROM*
  - *Tools generate ROM using embedded RAM & initialization file*
- *Requires constant explicitly defined for each choice in CASE statement*
- *May use **romstyle** synthesis attribute to control implementation*
- *Like RAMs, address or output must be registered to implement in Altera embedded RAM*

# Inferred ROM (Memory File)

```
module dp_rom (  
    output reg [7:0] q_a, q_b,  
    input [6:0] addr_a, addr_b,  
    input we, clk  
);  
  
reg [7:0] mem [0:127];  
  
initial  
    $readmemh("ram.dat", mem);  
  
always @ (posedge clk)  
begin  
    q_a <= mem[addr_a];  
    q_b <= mem[addr_b];  
end  
  
endmodule
```

- *Using \$readmemb or \$readmemh to initialize ram contents*
- *No write control*
- *Example shows dual-port access*
- *Automatically converted to ROM*
- *Tools generate ROM using embedded RAM & initialization file*



# Advanced Verilog Design Techniques

## *Coding State Machines*



# State Machine Coding

- Parameters or local parameters\* used to define states

```
parameter idle=0, fill=1, heat_w=2, wash=3, drain=4;
```

- Parameter “values” are replaced with state encoding values as chosen by synthesis tool
  - Use options/constraints in synthesis tool to control encoding style (e.g. binary, one-hot, safe, etc.)
- ``define` statements also supported, but not recommended

- Registers are used to store state


```
reg [2:0] current_state, next_state;
```

- Do not bit-slice `current_state` or `next_state` (e.g. `state[1:0]`)
- Separate sequential process from combinational process
- Sequential process should always include synchronous or asynchronous reset
- Use **case** statement to do the next-state logic, instead of **if-else** statement
  - Some synthesis tools do not recognize **if-else** statements for implementing state machines

*\* Discussed later*
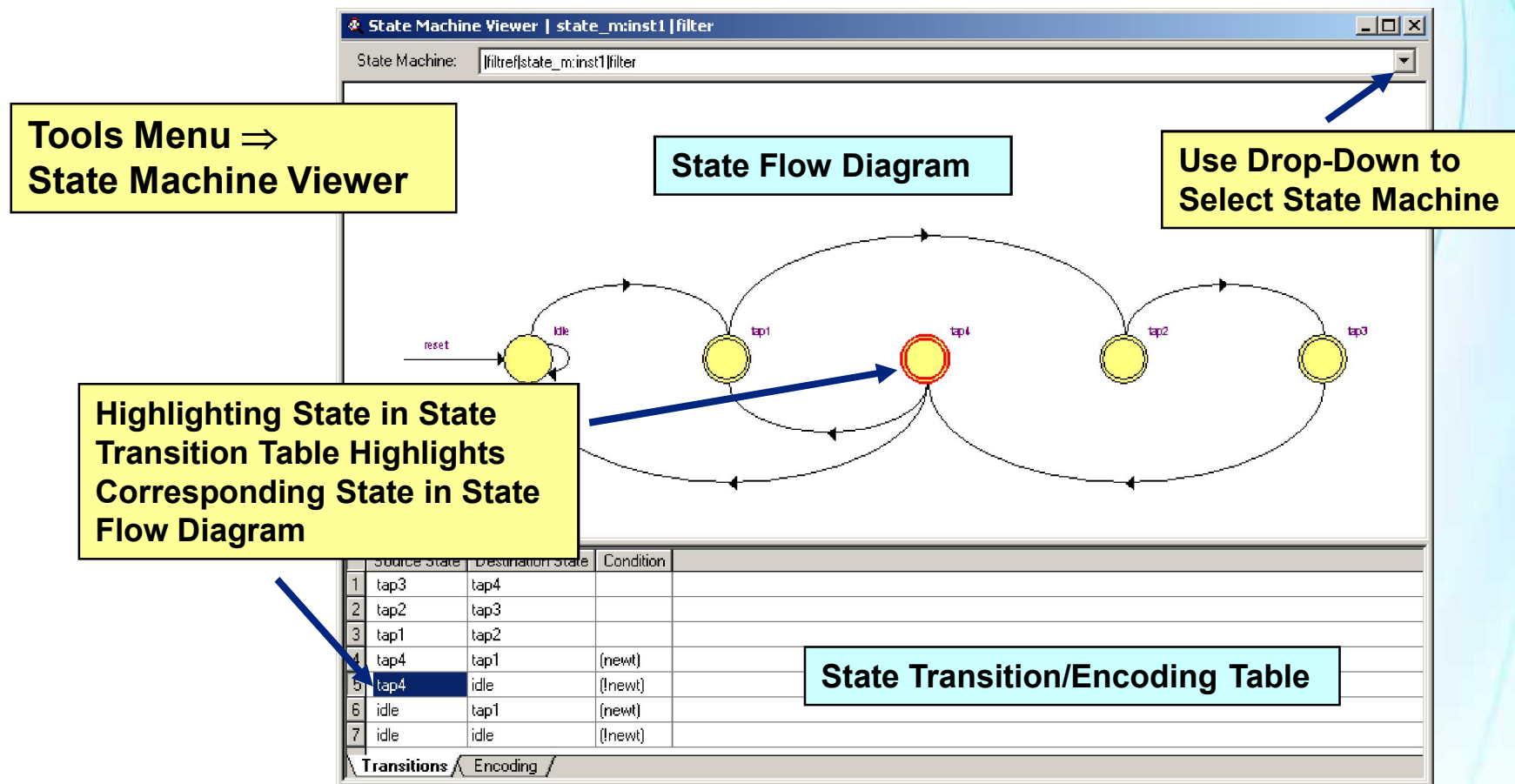
# State Machine Viewer

- Use to verify correct coding of state machine






# State Declaration

```
module state_machine (  
    input clk, reset, door_closed, full,  
    input heat_demand, done, empty,  
    output reg water, spin, heat, pump  
);
```

```
reg [2:0] current_state, next_state;
```

```
parameter idle=0, fill=1, heat_w=2, wash=3,  
    drain=4;
```

States

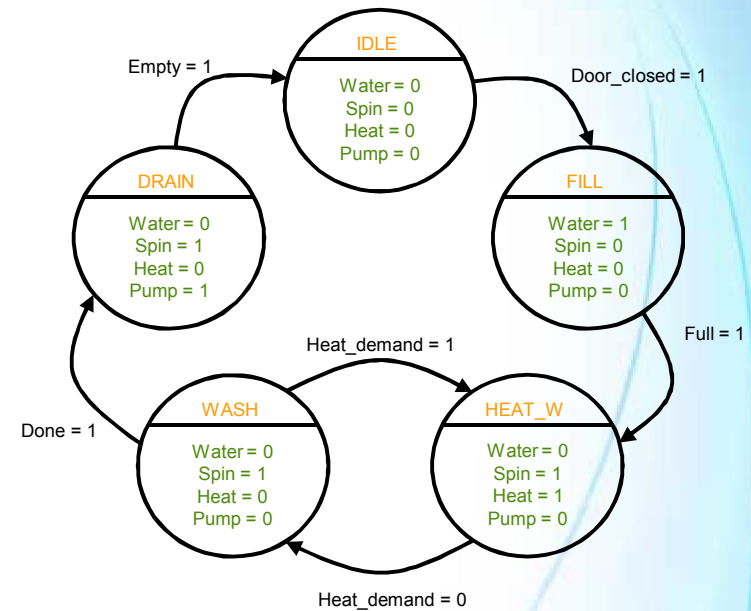

State Registers

# Next-State Logic

//State transitions


```
always @(posedge clk)
  if (reset)
    current_state <= idle;
  else
    current_state <= next_state;
```

*State transitions*

//Next State logic

```
always @ *
begin
  next_state = current_state; //default condition
  case (current_state)
    idle:    if (door_closed) next_state = fill;
    fill:    if (full) next_state = heat_w;
    heat_w:  if (heat_demand) next_state = wash;
    wash:    begin
              if (heat_demand) next_state = heat_w;
              if (done) next_state = drain;
            end
    drain:   if (empty) next_state = idle;
  endcase
end
```

*Next state logic*

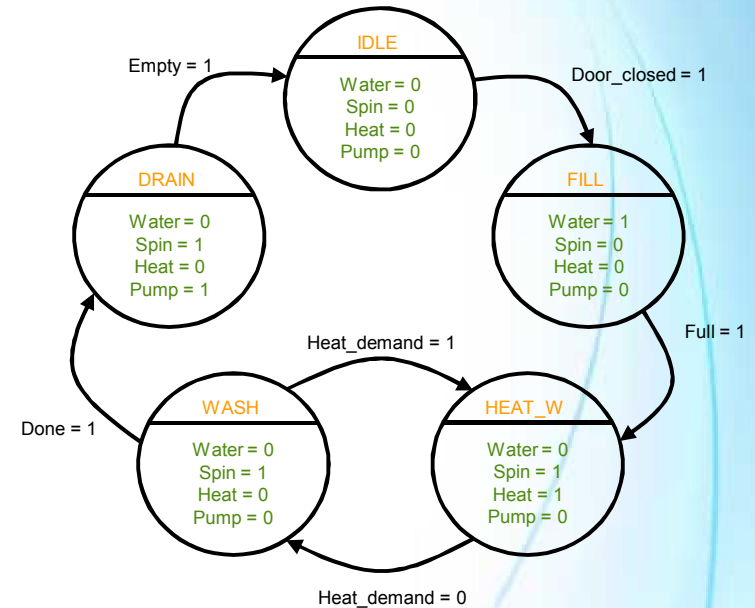




# Moore Combinatorial Outputs

```
//output logic
always @*
begin
    water = 0;
    spin = 0;
    heat = 0;
    pump = 0;
    case (current_state)
        idle:
            ;
        fill:
            water=1;
        heat_w:
            begin spin =1; heat = 1; end
        wash:
            spin =1;
        drain:
            begin spin =1; pump=1; end
    endcase
end
```


*Default output conditions*

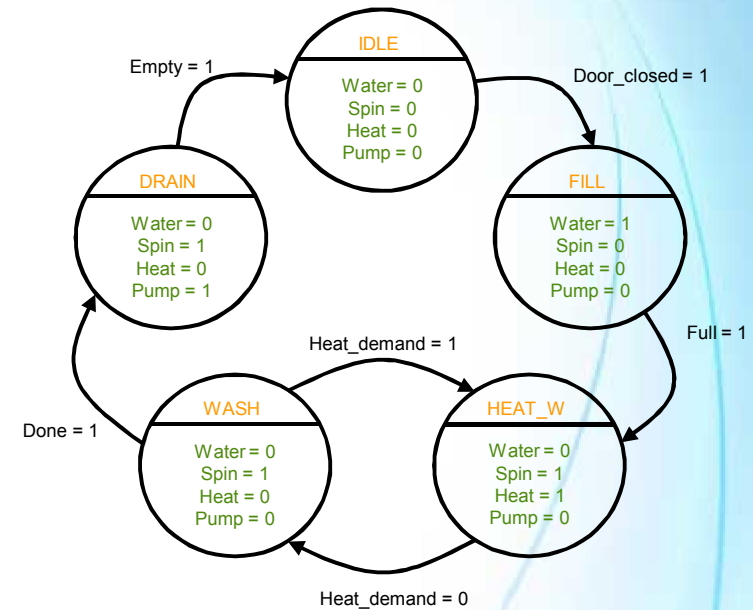

– Output logic function of state only
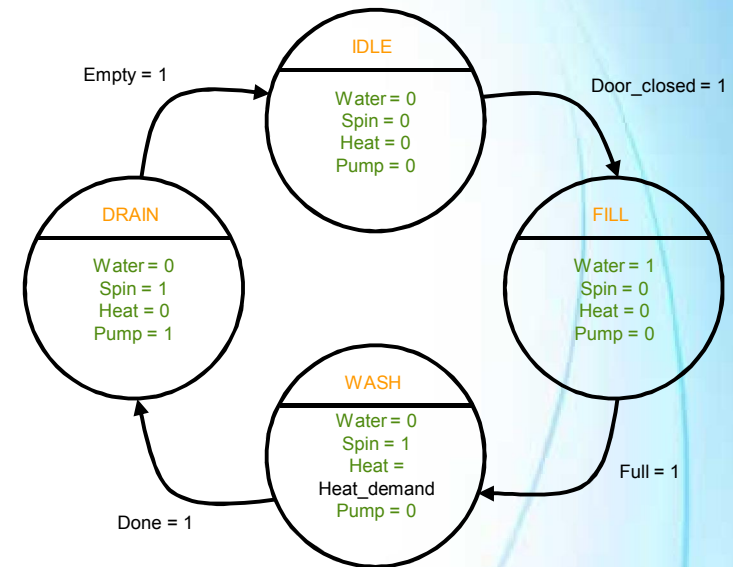
# Mealy Combinatorial Outputs

```
//output logic
always @ *
begin
  water=0;
  spin=0;
  heat=0;
  pump=0;
  case (current_state)
    idle:      ;
    fill:      water=1;
    wash:      begin spin =1; heat : 
    drain:     begin spin =1; pump: 
  endcase
end
```



– Output logic function of state only and input(s)

# State Machine Encoding Styles

State	Binary Encoding	Grey-Code Encoding	One-Hot Encoding	Custom Encoding
Idle	000	000	00001	?
Fill	001	001	00010	?
Heat_w	010	011	00100	?
Wash	011	010	01000	?
Drain	100	110	10000	?

- Quartus II default encoding styles for Altera devices
  - One-hot encoding for look-up table (LUT) devices
    - Architecture features lesser fan-in per cell and an abundance of registers
  - Binary (minimal bit) or grey-code encoding for product-term devices
    - Architecture features fewer registers and greater fan-in


# Undefined States

- Noise and spurious events in hardware can cause state machines to enter undefined states
- If state machines do not consider undefined states, it can cause mysterious “lock-ups” in hardware
- Good engineering practice is to consider these states
- To account for undefined states
  - Explicitly code for them (manual)
  - Use “safe” synthesis constraint (automatic)
 
# 'Safe' State Machine ??

```
//State transitions
always @(posedge clk)
    current_state <= next_state;


//Next State logic
always @ *
begin
    next_state = current_state; //default condition
    case (current_state)
        idle:    if (door_closed) next_state = fill;
        fill:    if (full) next_state = heat_w;
        heat_w:  if (heat_demand==0) next_state= wash;
        wash:    begin
                    if (heat_demand) next_state=heat_w;
                    if (done) next_state=drain;
                end
        drain:   if (empty) next_state=idle;
        default: next_state = idle;
    endcase
end
```



– Using default clause to cover all undeclared states


# Creating “Safe” State Machines

- Default clause does not make state machines “safe”
  - Once state machine is recognized, synthesis tool only accounts for explicitly defined states
  - Exception: Number of states equals power of 2 **AND** binary/grey encoding enabled
- Safe state machines created using synthesis constraints
  - Quartus II software uses
    - SAFE STATE MACHINE assignment applied project-wide and to individual FSMs
    - Verilog synthesis attribute
- May increase logic usage

	From	To	Assignment Name	Value	Enabled
1		 current_state	Safe State Machine	On	Yes
2	<<new>>	<<new>>	<<new>>		
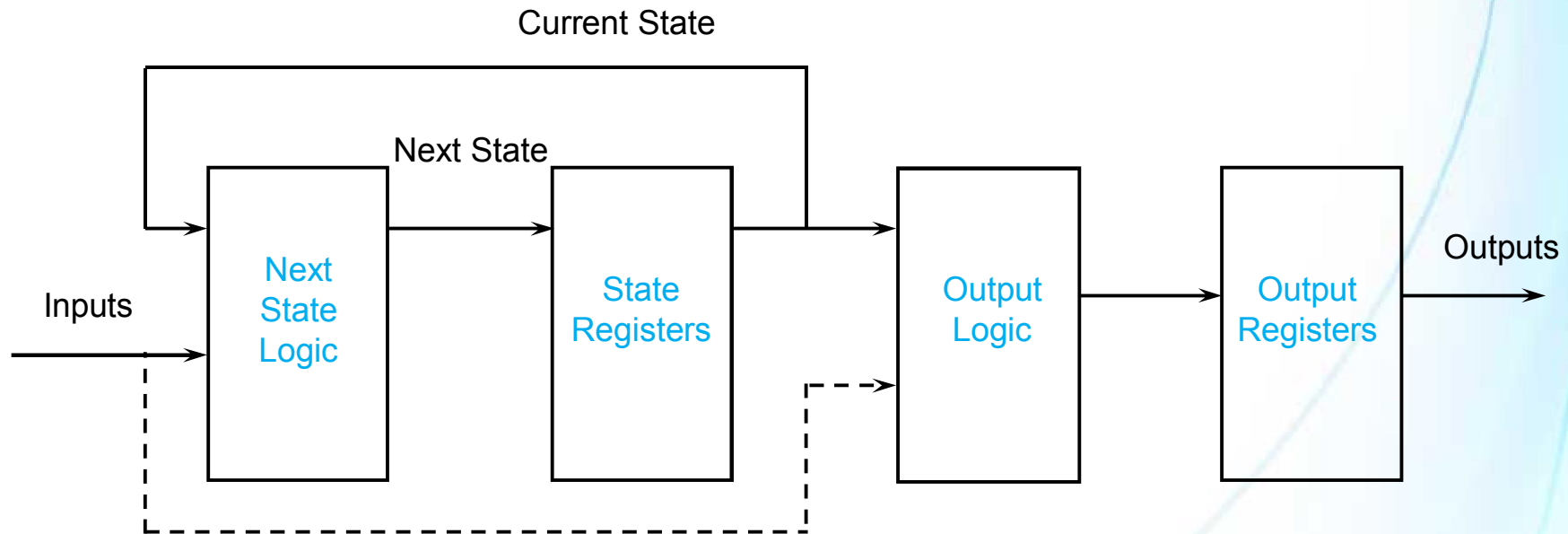
# Registered Outputs


- Remove glitches by adding output registers
  - Adds a stage of latency





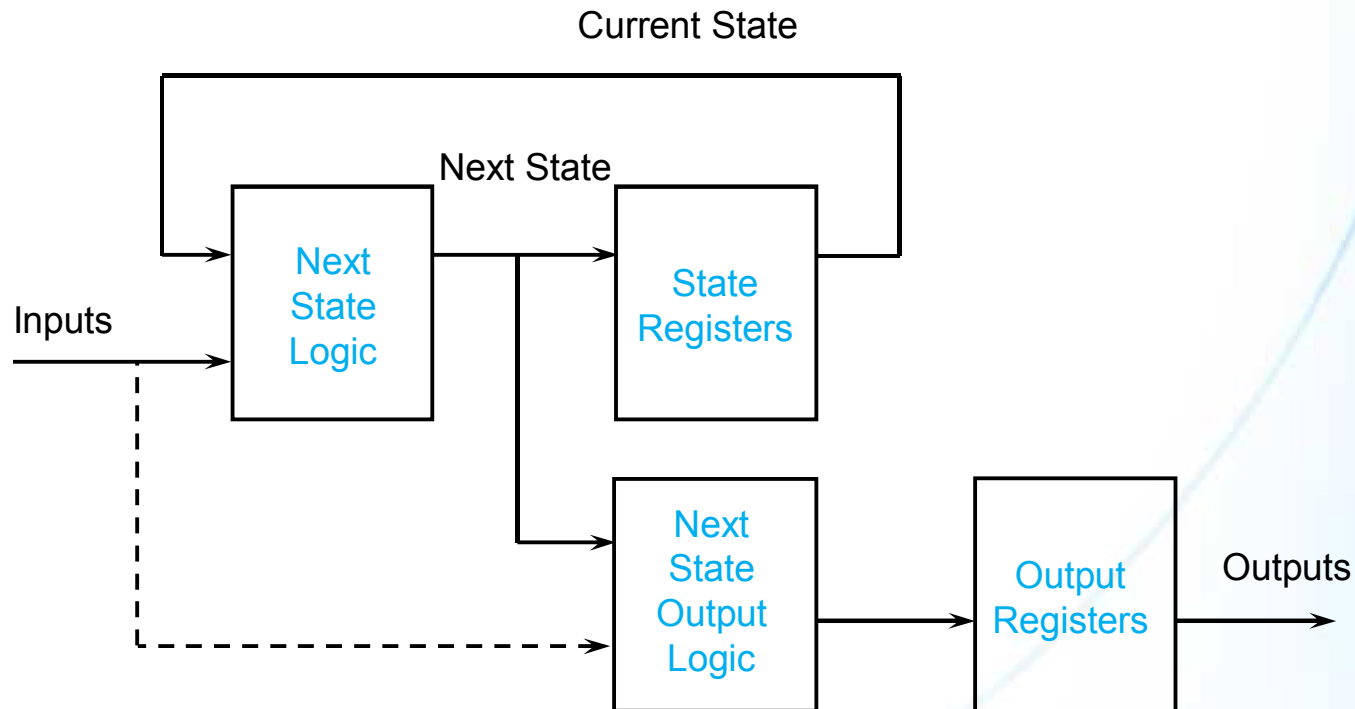
# Registered Outputs w/o Latency

- Base outputs on next state vs. current state
  - Output logic uses next state to determine what the next outputs will be
  - On next rising edge, outputs change along with state registers


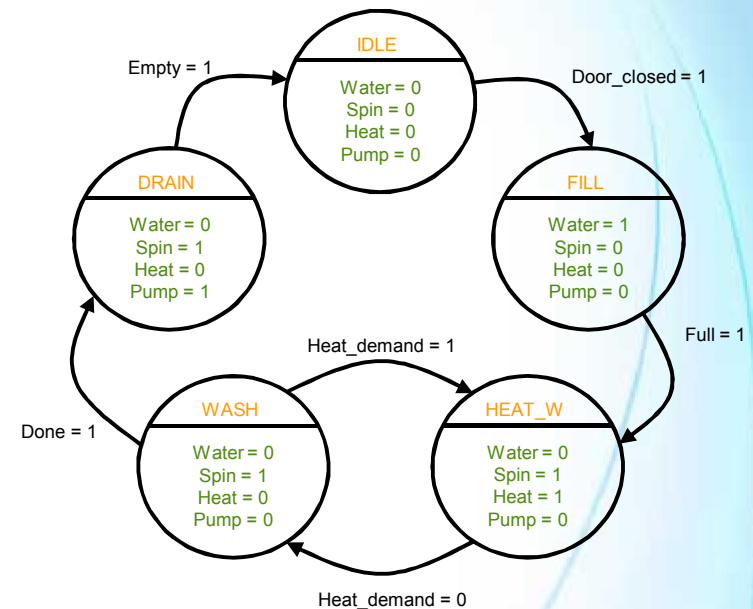
# Registered Outputs w/o Latency

```
//output logic
always @ (posedge clk)
begin
  water = 0;
  spin = 0;
  heat = 0;
  pump = 0;
  case (next_state)
    idle:      ;
    fill:      water <= 1;
    heat_w:    begin spin <= 1; heat <= 1; end
    wash:      spin <= 1;
    drain:     begin spin <= 1; pump <= 1; end
  endcase
end
```



- Base output logic case statement on next state variable (instead of current state variable)
- Wrap output logic with a clocked process

# Using Custom Encoding Styles

- Remove glitches without output registers
- Eliminate combinatorial output logic
- Outputs mimic state bits
  - Use additional state bits for states that do have exclusive outputs


State	Outputs	Custom Encoding
	Water Spin Heat Pump	
Idle	0 0 0 0	0000
Fill	1 0 0 0	1000
Heat_w	0 1 1 0	0110
Wash	0 1 0 0	0100
Drain	0 1 0 1	0101

# Custom State Encoding

```
reg [3:0] current_state, next_state;  
  
parameter idle = 'b0000, fill = 'b1000,  
            heat_w = 'b0110, wash = 'b0100,  
            drain = 'b0101;
```

*Custom Encoding*

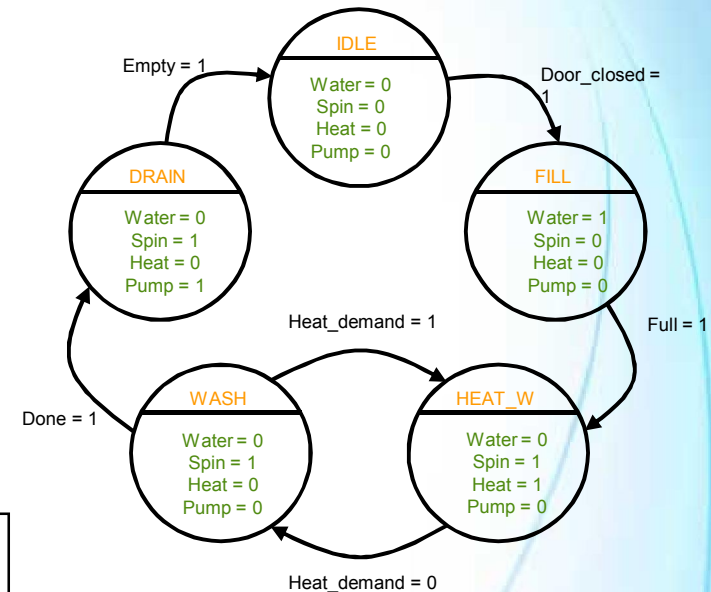- Must also set **State Machine Processing** assignment to **“User Encoded”**
- Output assignments are coded per previous examples (slides 83 or 84)
  - Synthesis automatically handles reduction of output logic
- Some tools use synthesis attributes like **enum\_encoding** OR **syn\_enum\_encoding** to perform custom state encoding



# Writing Efficient State Machines

- Remove counting, timing, arithmetic functions from state machine & implement externally
- Reduces overall logic & improves performance



# Advanced Verilog Design Techniques

*Improving Logic Utilization & Performance*



# Improving Logic Utilization & Performance

- Balancing Operators
- Resource Sharing
- Logic Duplication
- Pipelining



# Operators



- Synthesis tools replace operators with pre-defined (pre-optimized) blocks of logic
- Designer should control when & how many operators
  - Ex. Dividers
    - Dividers are large blocks of logic
    - Every '/' and '%' inserts a divider block and leaves it up to synthesis tool to optimize
    - Better resource optimization usually involves cleverly using multipliers or shift operations to do divide

# Generating Logic from Operators



- Synthesis tools break down code into logic blocks
- They then assemble, optimize & map to hardware

```
if (sel < 10)
    y = a + b;
else
    y = a + 10;
```


1 Comparator

  

2 Adders

  

1 Multiplexer

 


# Balancing Operators

- Use parenthesis to define logic groupings
  - Increases performance & utilization
  - Balances delay from all inputs to output
  - Circuit functionality unchanged


## Unbalanced

$$\text{out} = a * b * c * d;$$

 

## Balanced

$$\text{out} = (a * b) * (c * d);$$

 


# Balancing Operators: Example

- a, b, c, d: 4-bit vectors


## Unbalanced

$$\text{out} = a * b * c * d$$

 

## Balanced

$$\text{out} = (a * b) * (c * d)$$

 


# Resource Sharing

- Reduces number of operators needed
  - Reduces area
- Two types
  - Sharing operators among mutually exclusive functions
  - Sharing common sub-expressions
- Synthesis tools can perform automatic resource sharing
  - Feature can be enabled or disabled
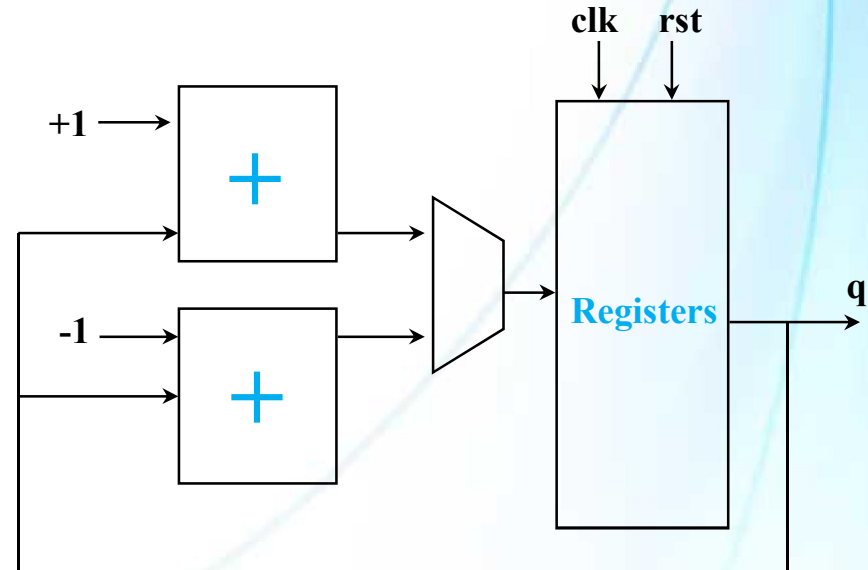
# Mutually Exclusive Operators

```
module test (  
    input rst, clk, updn,  
    output [7:0] q,  
    reg [7:0] q  
);  
  
always@(posedge clk, negedge rst)  
begin  
    if (!rst)  
        q<=0;  
    else if (updn)  
        q <= q + 1;  
    else  
        q <= q - 1;  
end  
endmodule
```

- Up/down counter
- 2 adders are mutually exclusive & can be shared (typically if-else with same operator in both choices)




# Sharing Mutually Exclusive Operators

```
module test (  
    input rst, clk, updn,  
    output reg [7:0] q  
);  
  
always @ (posedge clk, negedge rst) begin  
    if (!rst)  
        q <= 0;  
    else  
        q <= q + ( updn ? 1 : -1);  
    end  
endmodule
```

*Single add operation*

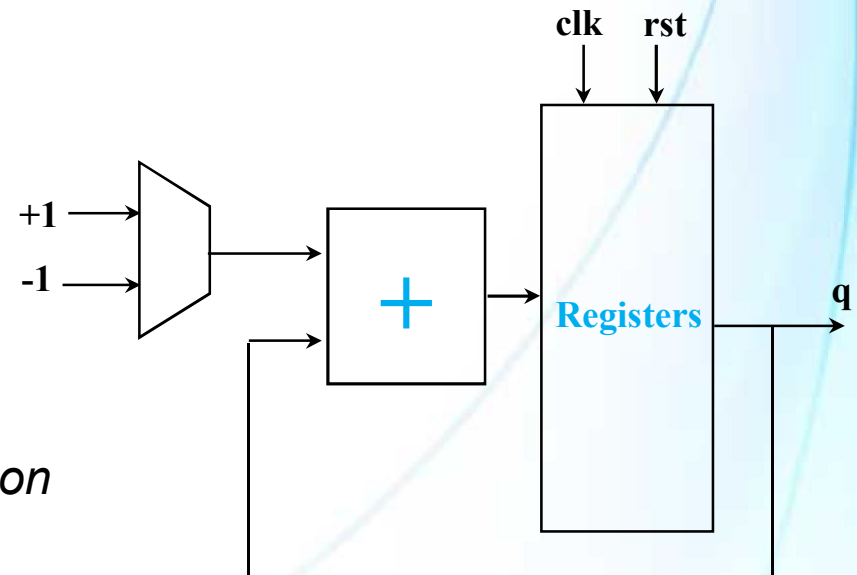- *Up/down counter*
- *Only one adder required*






# How Many Multipliers?

$$y = a * b * c$$
$$z = b * c * d$$

# How Many Multipliers? (Answer)

$$y = a * b * c$$
$$z = b * c * d$$

 


4 Multipliers!

# How Many Multipliers Again?

$$y = a * (b * c)$$
$$z = (b * c) * d$$

## How Many Multipliers Again? (Answer)

$$y = a * (b * c)$$
$$z = (b * c) * d$$

 

3 Multipliers!


- This is called sharing common subexpressions
- Some synthesis tools do this automatically, but some don't!
- Parentheses guide synthesis tools
- If  $(b*c)$  is used repeatedly, assign to temporary signal

# Logic Duplication

- Intentional duplication of logic to reduce fan-out
- Synthesis tools can perform automatically
  - User sets maximum fan-out of a node

 
# Fan-Out Problems

- High fan-out increases placement difficulty
  - High fan-out node cannot be placed close to all destinations
  - Ex: Fan-out of 1 & 15


 
# Controlling Fan-Out


- By replicating logic fan-out can be reduced
  - Worst case path now contains fan-out 3 and 5




 
# Logic Duplication Example

- High fan-out node duplicated & placed to reduce delay



# Automatic Fan-Out Control


- Most synthesis tools feature options which limit fan-out
- Advantage: Easy experimentation
- Disadvantage: Less control over results
  - Knowing which nodes have high fan-out & their destination helps floor-planning

# Shift Register example

```


module test (
    input clk, sclr_in, shiftin,
    output shiftout
);
reg [63:0] rega, regb, regc;
reg sclr;
always @(posedge clk)
    sclr <= sclr_in;
always @(posedge clk) begin
    if (sclr)
        regc <= 0;
    else
        regc <= {regc[62:0], regb[63]};
    if (sclr)
        regb <= 0;
    else
        regb <= {regb[62:0], rega[63]};
    if (sclr)
        rega <= 0;
    else
        rega <= {rega[62:0], shiftin};
end
assign shiftout = regc[63];
endmodule

```

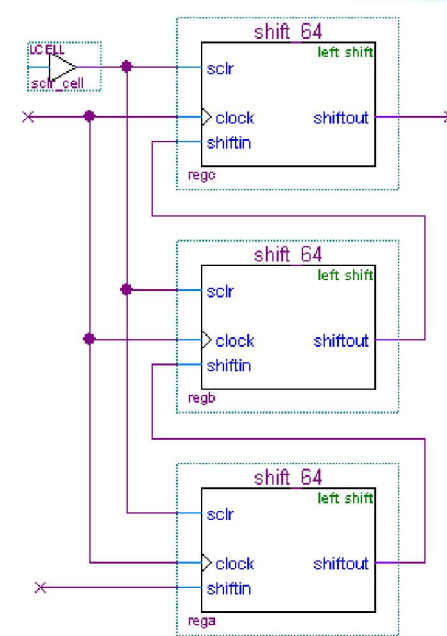

- *sclr fans out to each DFF within 3 64 bit shift registers*
- *The shift registers are cascaded to produce one 192 bit shift register*
- *sclr provides a synchronous clear function*

# Fan-Out to 192 Registers

 


© 2009 Altera Corporation—**Confidential**

ALTERA, ARRIA, CYCLONE, HARDCOPY, MAX, MEGACORE, NIOS, QUARTUS & STRATIX are Reg. U.S. Pat. & Tm. Off. and Altera marks in and outside the U.S.

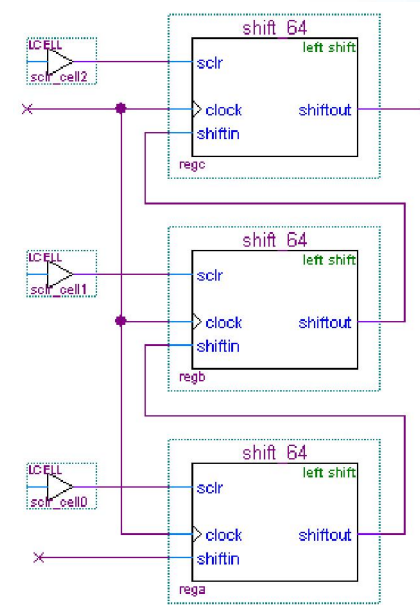
# Shift Register with Reduced Fan-Out

```
always @(posedge clk) begin
  if (sclr2)
    regc <= 0;
  else
    regc <= {regc[62:0], regb[63]};
  if (sclr1)
    regb <= 0;
  else
    regb <= {regb[62:0], rega[63]};
  if (sclr0)
    rega <= 0;
  else
    rega <= {rega[62:0], shiftin};
end
assign shiftout = regc[63];
```



- *sclr is replicated so that it appears 3 times*
- *Fan-out from the previous cell has gone from 1 to 3 but this is insignificant*

# Fan-Out to 64 Registers

 

© 2009 Altera Corporation—**Confidential**



ALTERA, ARRIA, CYCLONE, HARDCOPY, MAX, MEGACORE, NIOS, QUARTUS & STRATIX are Reg. U.S. Pat. & Tm. Off. and Altera marks in and outside the U.S.

# Pipelining

- Purposefully inserting register(s) into middle of combinatorial data (critical) path
- Increases clocking speed
- Adds levels of latency
  - More clock cycles needed to obtain output
- Some tools perform automatic pipelining
  - Same advantages/disadvantages as automatic fan-out



# Adding Single Pipeline Stage

 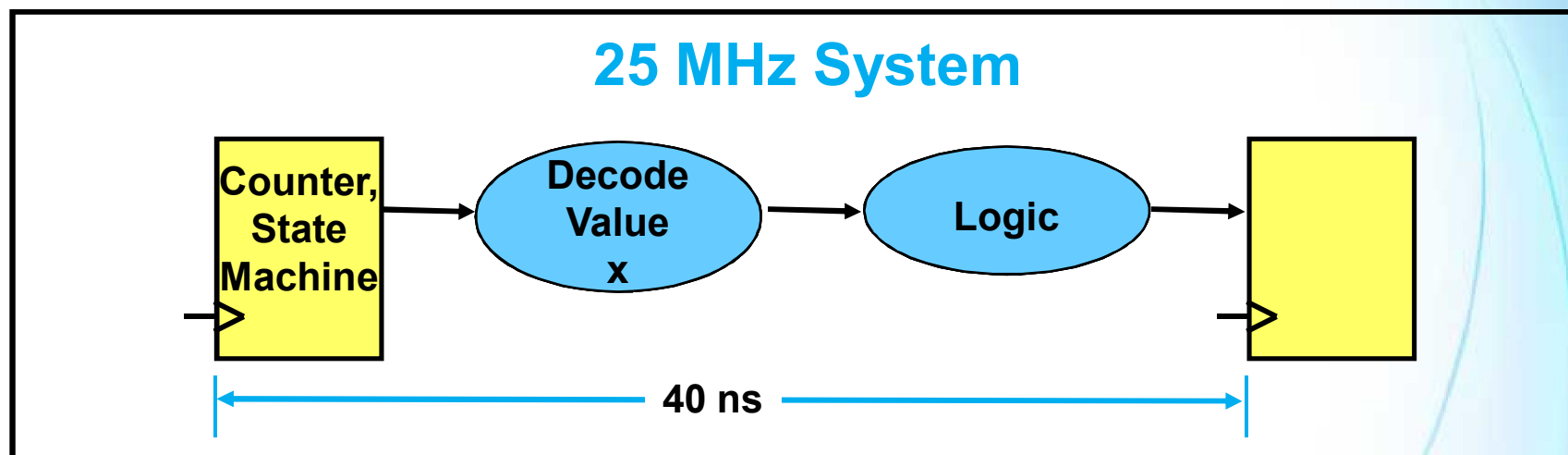

# Adding Single Pipeline Stage in Verilog


## Non-Pipelined

```
module test (  
    input clk, clr_n,  
    input [7:0] a, b, c, d,  
    output reg [31:0] result  
);  
reg [7:0] atemp, btemp, ctemp, dtemp;  
  
always @(posedge clk, negedge clr_n)  
begin  
    if (!clr_n) begin  
        atemp <= 0;  
        btemp <= 0;  
        ctemp <= 0;  
        dtemp <= 0;  
        result <= 0;  
    end else begin  
        atemp <= a;  
        btemp <= b;  
        ctemp <= c;  
        dtemp <= d;  
        result <= (atemp * btemp) * (ctemp * dtemp);  
    end  
end  
endmodule
```

## Pipelined

```
module test (  
    input clk, clr_n,  
    input [7:0] a, b, c, d,  
    output reg [31:0] result  
);  
reg [7:0] atemp, btemp, ctemp, dtemp;  
reg [15:0] int1, int2;  
  
always @(posedge clk, negedge clr_n)  
begin  
    if (!clr_n) begin  
        atemp <= 0;  
        btemp <= 0;  
        ctemp <= 0;  
        dtemp <= 0;  
        int1 <= 0;  
        int2 <= 0;  
        result <= 0;  
    end else begin  
        atemp <= a;  
        btemp <= b;  
        ctemp <= c;  
        dtemp <= d;  
        int1 <= atemp * btemp;  
        int2 <= ctemp * dtemp;  
        result <= int1 * int2;  
    end  
end  
endmodule
```

# Pipelined 4-Input Multiplier

 



# Advanced Verilog Design Techniques

## *Introduction to Testbenches*



# Purpose of Testbench

- Generate stimulus to test design for normal transactions, corner cases and error conditions
  - Direct tests
  - Random tests
- Automatically verify design to spec and log all errors
  - Regression tests
- Log transactions in a readable format for easy debugging

# Three Classes of Traditional Testbenches

- I. Test bench applies stimulus to target code and outputs are manually reviewed
- II. Test bench applies stimulus to target code and verifies outputs functionally
  - Requires static timing analysis
- III. Test bench applies stimulus to target code and verifies outputs with timing
  - Does not require full static timing analysis
  - Code and test bench data more complex
  - Not covered


# Advantages/Disadvantages

Testbench Type	Advantages	Disadvantages	Recommendation
Class I	<ul style="list-style-type: none"> <li>• Simple to write</li> </ul>	<ul style="list-style-type: none"> <li>• Requires manual verification</li> <li>• Takes longer for others (not original designer) to verify</li> <li>• Easy for others to miss errors</li> </ul>	<ul style="list-style-type: none"> <li>• Great for verifying simple code</li> <li>• Not intended for re-use</li> </ul>
Class II	<ul style="list-style-type: none"> <li>• Easy to perform verification once complete</li> <li>• “Set and forget it”</li> </ul>	<ul style="list-style-type: none"> <li>• Takes longer to write</li> <li>• More difficult to debug initially</li> </ul>	<ul style="list-style-type: none"> <li>• Better for more complicated designs, designs with complicated stimulus/outputs and higher-level designs</li> <li>• Promotes re-usability</li> </ul>
Class III	<ul style="list-style-type: none"> <li>• Most in-depth</li> <li>• “Guarantees” design operation, if successful (subject to model accuracy)</li> </ul>	<ul style="list-style-type: none"> <li>• Takes longest to write</li> <li>• Most difficult to debug</li> <li>• Physical changes (i.e. target device, process) requires changing testbench</li> </ul>	<ul style="list-style-type: none"> <li>• Might be overkill for many FPGA designs</li> <li>• Required for non-Altera ASIC designs</li> </ul>


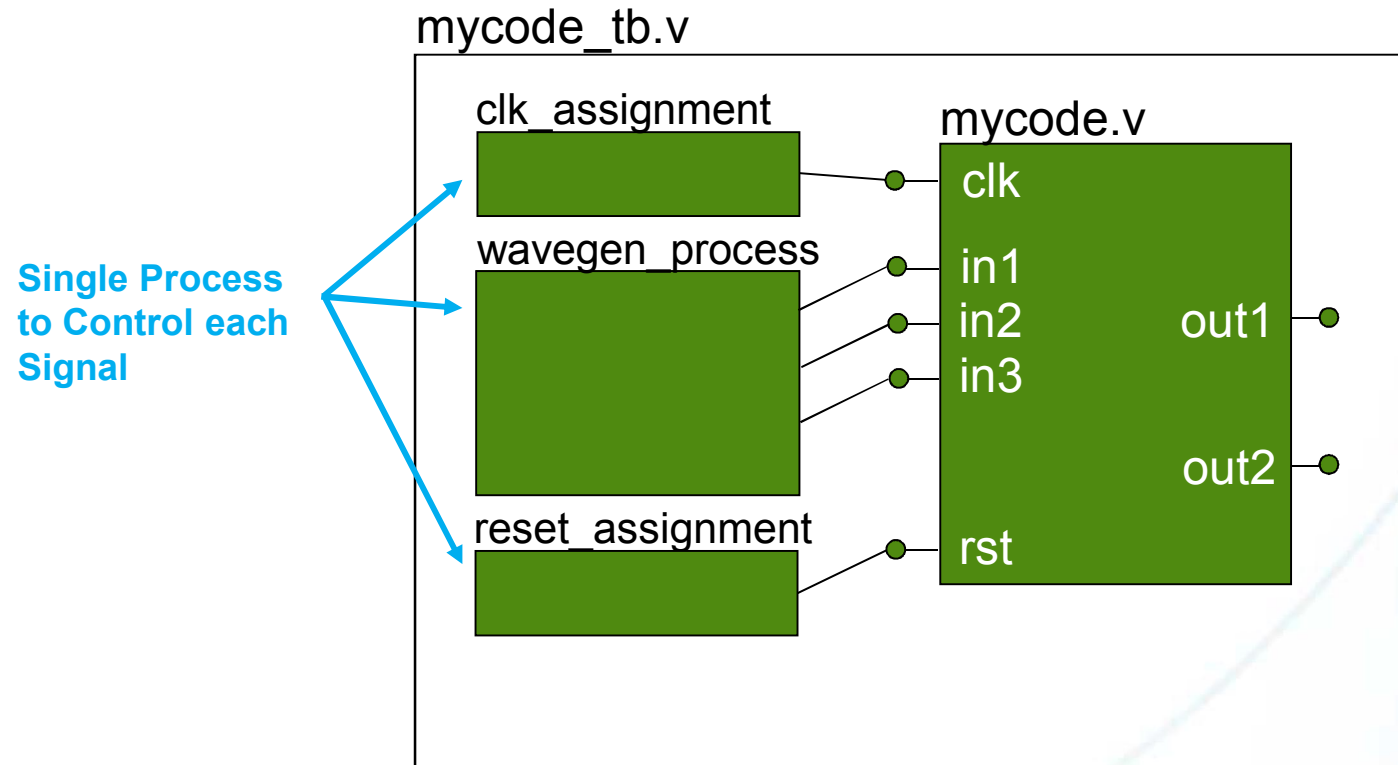
# General Class I Methods

- Create “test harness” code to instantiate the device under test (DUT) or target code
- Create stimulus signals to connect to DUT




# Test Vector Generation

- Develop sequence of fixed input values
- Test vector development from bottom up
  - Write basic tasks
  - Write more complex tasks based on basic tasks
  - Perform tests
- Example – memory testing
  - Basic tasks: readmem, writemem
  - 2<sup>nd</sup> level tasks: initmem, copymem, comparemem
  - Generation of tests based on tasks
 
# Concurrent Statements

- Signals with regular or limited transitions can be created with separate *initial* blocks (concurrent statements)
- These statements can begin a testbench and reside outside any other processes



# Example Initial Blocks

```
`timescale 1ns / 1ns
`define CLKPERIOD 20
module tb();

reg clk;
reg resetn;

initial // Clock procedural block
begin
    clk = 0;
    forever clk = #(`CLKPERIOD/2) ~clk;
end

initial // Reset procedural block
begin
    resetn = 1;
    #20 resetn = 0;
    #20 resetn = 1;
end


initial #2500 $stop;

endmodule
```

- Use **initial** blocks to define
- Initial block tells the simulator to run the code at time zero
- Code continues running until all statements finish

Clock Process

Reset Process

 

# Creating Periodic Signals

```
`timescale 1ns / 1ns
`define CLKPERIOD 30
module count_gen_tb();

reg clk;
reg [7:0] bus, count;

initial clk=0;

always #(`CLKPERIOD/2) clk=(clk !== 1?1:0);

initial
begin: count_gen
    count = 0;
    bus = 0;
    forever begin
        repeat (2) @(posedge clk) ;
        bus = count;
        count = count + 1;
    end
end

initial #2500 disable count_gen;

endmodule
```

- Use separate initial or always blocks to create more periodic stimulus

- Initial blocks more common

- ***Initial** and **always** blocks to define free-running clock*
  - *Second **initial** block (count\_gen) with forever loop to input counting pattern (every other clock edge)*
  - *Third **initial** block uses **disable** statement to turn off counting pattern after 2500 ns*

# Working with Delay

```
`timescale 1ns / 1ns
`define CLKPERIOD 30
module tb();

reg clk;
reg reset;

initial
begin
    clk = 0;
    forever clk = #(`CLKPERIOD/2) ~clk;
end

initial
begin
    reset = 1;
    #20 reset = 0;
    #20 reset = 1;
end

initial #2500 $stop;

endmodule
```

*Define the time scale & precision*

*Define a clock period*

## ■ Defining a timescale

- Choose the largest precision that can accurately model the system
  - Too small of a precision can needlessly increase memory usage and simulation time
- Timescale passed to all modules without defined timescales that are subsequently elaborated
  - Simulator warning

## ■ Defining clock period(s)

- Place in top level test bench module or in a “definitions” header file that is included from top

## ■ Use blocking assignments and regular assignment delay for specifying stimulus


- Simulate faster and use less memory than non-blocking
- Non-blocking assignments with intra-assignment delay can be used to model delay lines

# Simple Verilog Class I Testbench

<pre>`timescale 1 ns/1 ns module addtest();</pre>	← Top-level entity has no ports
<pre>parameter CLKPERIOD = 20; parameter PERIOD = 60; reg [3:0] a,b; wire [3:0] sum; reg clk;</pre>	← Signals to assign values & observe
<pre>adder add1(.clk(clk), .a(a), .b(b), .sum(sum));</pre>	← Instantiate lower-level entity
<pre>initial clk = 1'b0;  always #(CLKPERIOD/2) clk=(clk != 1?1:0);</pre>	← Create clock to synchronize actions
<pre>initial begin: adder_stim   @(negedge clk) ;   a = 3'b0;    b = 3'b0;   #PERIOD ;   forever begin     @(negedge clk) ;     a = a + 3'd2;     b = b + 3'd3;     #PERIOD ;   end end  initial #1000 \$stop;  endmodule</pre>	← Apply stimulus; Note input data changing only on inactive clock edge




# Example Results

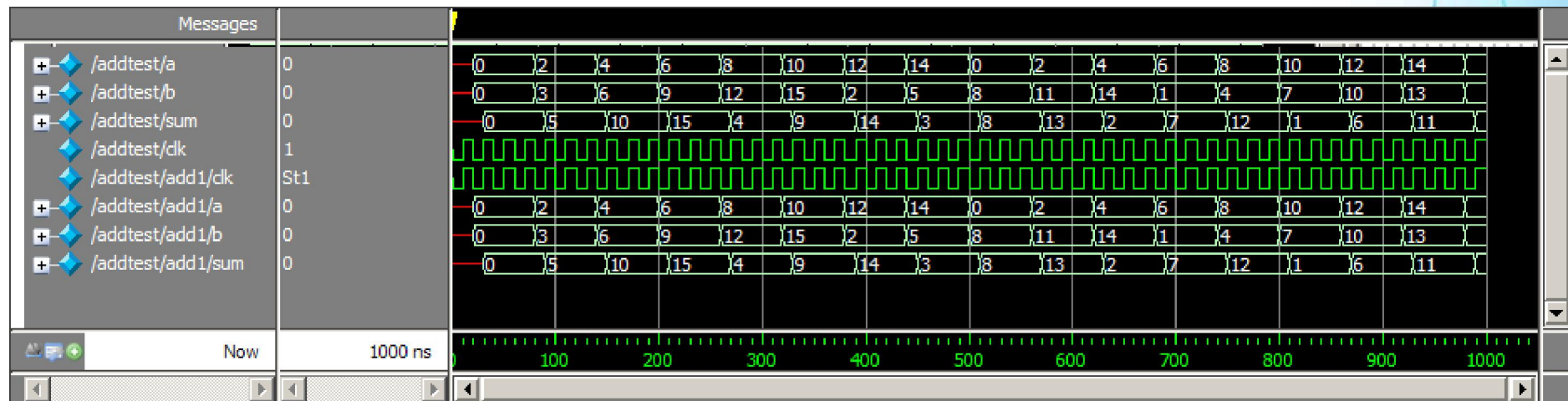
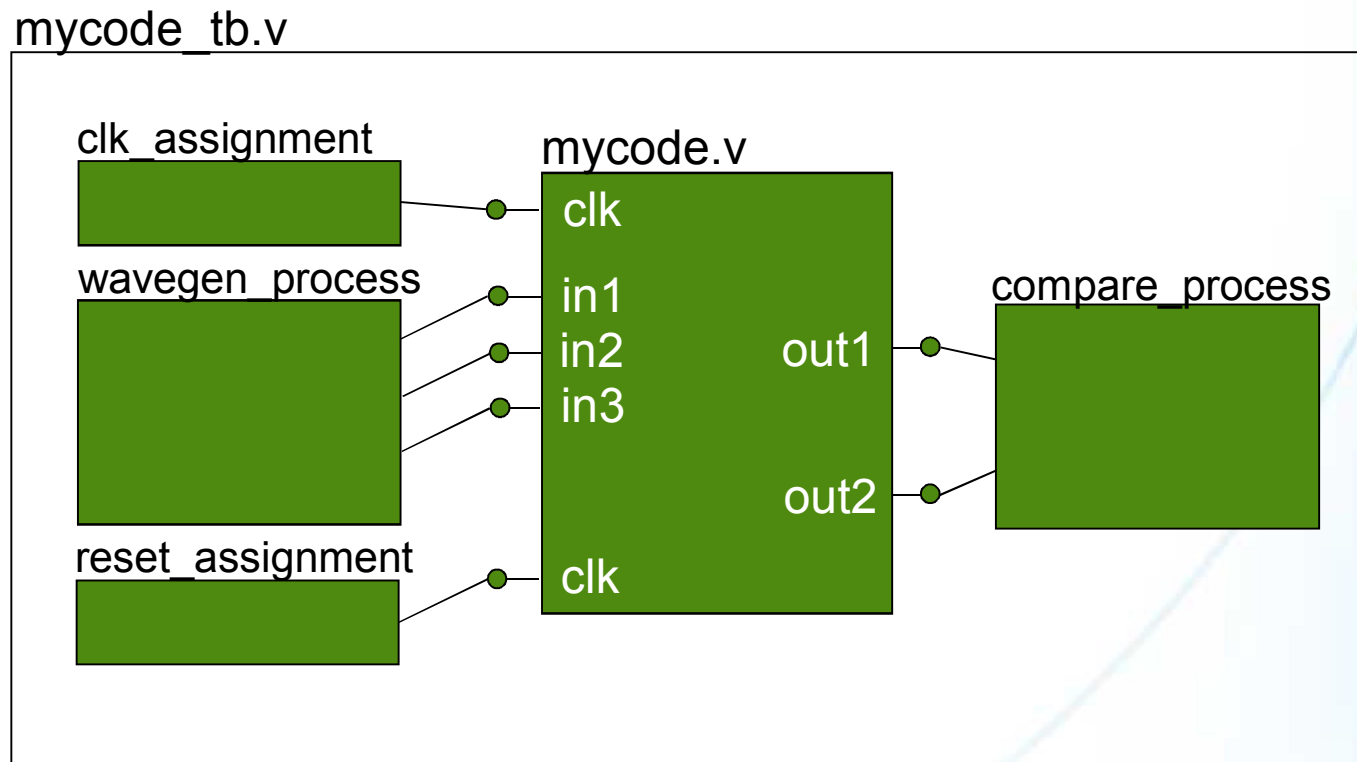
## Class II (& III) Methods

- Add a compare process to an existing design so that outputs can be monitored



# Self Verification Methods

- May use a “compare process” to check received results against expected results
- Single simulation can use one or multiple testbench files
  - Single testbench file containing all stimulus and all expected results
  - Multiple testbench files based on stimulus, expected results or functionality (e.g. data generator, control stimulus)
- Many times signaling is too complicated to model without using vectors saved in “time-slices”

# Simple Self Verifying Test Benches

```
adder add1(.clk(clk), .a(a), .b(b), .sum(sum));
```

```
initial begin
```

```
    @ (negedge clk) ;
```

```
    a = 0; b = 0;
```

```
    #40 if (sum !== 0) begin
```

```
        $display("Sum is wrong");
```

```
        $display("Expected 0, but received %d",  
                sum);
```

```
    $finish;
```

```
end
```

```
    @ (negedge clk) ;
```

```
    a = a + 3'd2; b = b + 3'd3;
```

```
    #40 if (sum !== 5) begin
```

```
        $display("Sum is wrong");
```

```
        $display("Expected 5, but received %d",  
                sum);
```

```
    $finish;
```

```
end
```

```
    // Repeat above varying values of a and b
```

```
end
```

```
end
```

- Code repeated for each test case
- Result checked

- Simple self verifying test bench
- Each block checks for correct answer
  - Minimizes human error
- Code not very efficient
  - Each test case requires a lot of repeated code
- Improve this code by introducing a task

# Simplify Test Bench with Task

```
adder add1(.clk(clk), .a(a), .b(b), .sum(sum));
```

```
initial begin
```

```
    test(0, 0, 0);  
    test(2, 3, 5);  
    test(4, 6, 10);  
    test(6, 9, 15);  
    test(8, 12, 4);  
    test(10, 15, 9);  
    $finish ;
```

```
end
```

```
task test;
```

```
    input [3:0] in_a, in_b, exp_result;  
    begin  
        @(negedge clk) ;  
        a = in_a;  
        b = in_b;  
        #40 if( sum !== exp_result) begin  
            $display("Result is wrong");  
            $display("Expected %d, but received %d",  
                exp_result, sum);  
            $finish;  
        end  
    end
```

```
end  
endtask
```

- Task used to simplify test bench

- Task improves efficiency and readability of testbench
- Advantage: Easy to write
- Disadvantages
  - Each task execution (like last example) assigns values to a, b then waits to compare sum to its predetermined result
  - Very difficult to do for complicated signaling

# Storing Stimulus/Results in “Time Slices”

- Write stimulus/results into text files
  - e.g. Store one time slice per line (all inputs or expected outputs separated by spaces)
- Read stimulus and expected results into Verilog memory arrays inside test bench
  - Use the *\$readmemh* or *\$readmemb* system tasks to read external files into a Verilog arrays (discussed earlier)



# Example Test Bench Using Text Files & Memories

```

module addtest_mem_tb;
reg [3:0] input_mem [0:13]; // Memory to hold input stimulus
reg [3:0] exp_mem [0:6]; // Memory to hold expected results
reg [3:0] a, b, exp_result;
wire [3:0] sum;
reg clk;
integer i;

initial begin //Initialization block
    clk = 1'b0;
    $readmemb("init.dat", input_mem); // Read input stimulus into memory
    $readmemb("exp.dat", exp_mem); // Read expected output results into memory
end

always #10 clk=(clk !== 1?1:0); //Define system clock

//Instantiate the device under test (dut)
adder add1 (.clk(clk), .a(a), .b(b), .sum(sum));

initial begin
    for (i=0; i< 7; i = i+1) begin // Loop through memory values
        @(negedge clk) ; // Drive inputs on inactive clock edge

        a = input_mem[2*i]; // Read 2 values from input stimulus memory to
        b = input_mem[(2*i)+1]; // be driven into dut

        exp_result = exp_mem[i]; // Read 1 value from expected outputs memory

        @(negedge clk) ; //perform checking on next falling edge clock
        if (exp_result !== sum) // Compare dut result against expected result
            $display("%0d : Calculated %0d, Expected %0d", // & print to display
                $time, sum, exp_result);
    end
end
endmodule
    
```

- This example uses 1 data file/memory for input stimulus & one data file/memory for expected results
- For loop used to loop through all stimulus and expected results memories
  - Be careful of stimulus files being shorter than memories
- Note that more complex operation would require more complicated stimulus (e.g. output qualifier signal, input stimulus and output checking in separate procedural blocks, separate memories per data input)



# Example Input Memory Files

*init.dat*

// a_in	b_in
@000	
0000	0000
@004	
0010	0011
0100	0110
0110	1001
1000	1100
1010	1111

*exp.dat*

0000
XXXX
0101
1010
1111
0100
1001

- *Each value separated by white space read into separate memory address*
- *Both \$readmemb and \$readmemh treat all types of white spaces (e.g. spaces, new line characters, tabs) identically*

# Example Test Plan

- Develop high-level behavioral (i.e. non-synthesizable) model of design
- Create stimulus/test vectors to simulate model
- Generate expected results from behavioral model simulation
- Replace behavioral blocks with RTL model blocks
  - Simulate each RTL block with other behavioral blocks to ensure functionality is the same



# Advanced Verilog Design Techniques

## *Parameterized Code*



# Parameterized Code

- Writing code to enable reuse and flexibility
  - Logic blocks that are made scalable
  - Different configurations of same model
- 2 Verilog constructs support parameterization
  - Parameters
  - Constant function
  - Generate constructs
    - If
    - Case
    - Loop

# Parameters (Review)

- Module constants used to pass information to an instance
  - Scalable code
  - Changing module behavior
- Must resolve to a constant at compile time

```
module reg_bank
    // Parameter defaults to 1, but can be overridden
    (
        ;
        .
        .
        .
    endmodule
```

# Parameterized Counter

```
module counter is
```

```
(
```

```
);
```

```
always @ (posedge clk or posedge clr)
```

```
    if (clr)
```

```
        q <= 0;
```

```
    else if (sload)
```

```
        q <= data;
```

```
    else if (cnt_en)
```

```
        q <= q + 1;
```

```
endmodule
```

Parameter  
WIDTH used to  
scale counter

– *Parameter set to default value to  
make optional*




# Instantiating a Parameterized Module

- Must map to parameters & ports in instantiation
- Generic & port resolution done at compile time
- Default parameters overridden if explicitly defined
  - Specified 16 overrides default 8
  - No need to specify a parameter in instantiation if using its default
- Unconnected outputs leave empty <.q (> or omit completely
- Set unused inputs to correct active/inactive value

```
counter # (.WIDTH(16))  
  u1 (.clk(tclk), .clr(tclr),  
      .cnt_en(tcnt_en),  
      .sload(1'b0),  
      .data(16'b0),  
      .q(tq));
```

*Inactive value for sload*

 



# Complete Code

```
module top_counter
(
  input tclk, tclr, tcnt_en,
  output reg [15:0] tq
);

  counter #(.WIDTH(16))
    u1 (.clk(tclk), .clr(tclr),
        .cnt_en(tcnt_en),
        .sload(1'b0),
        .data(16'b0),
        .q(tq));
endmodule
```

- *This instantiation method for parameters introduced in Verilog-2001 and is the most explicit and easy to read*
  - *Other methods supported*
  - *May require explicitly defining all parameters even if defaults are used*
  - *Using defparams not recommended*

# Local Parameters

- Verilog-2001 enhancement
- Parameter that cannot be redefined during instantiation
  - Base local parameters on parameters
  - Protects parameters from accidental redefinition
- Cannot be used in module definition

```
module memory
    #(parameter D_WIDTH = 8,
        A_WIDTH = 4)
    (
        input clk, we,
        input [A_WIDTH-1:0] addr,
        input [D_WIDTH-1:0] data,
        output reg [D_WIDTH-1:0] q
    );
    localparam M_DEPTH = 2**A_WIDTH;
    reg [D_WIDTH-1:0] mem [0:M_DEPTH-1];
    always @ (posedge clk)
    begin
        if (we)
            mem[addr] <= data;
            q <= mem[addr];
    end
endmodule
```

# Constant Functions

```
module ram_const_func
  #(parameter D_WIDTH = 8, RAM_DEPTH = 2048)
  (
    output reg [D_WIDTH-1:0] q,
    input [D_WIDTH-1:0] d,
    input [clogb2(RAM_DEPTH)-1:0] addr,
    input we, clk
  );

  function integer clogb2 (
    input integer mem_depth
  );
    begin
      for (clogb2 = 0; mem_depth > 0;
          clogb2 = clogb2 + 1)
        mem_depth = mem_depth >> 1;
      end
    endfunction

  reg [7:0] mem [0:RAM_DEPTH];

  always @(posedge clk)
  begin
    if (we)
      mem[addr] <= d;
    q <= mem[addr];
  end

endmodule
```

*Constant Function call  
used to determine  
address width*

*Constant function  
**clogb2** definition*

- Functions whose result evaluates to a constant at elaboration time
- Adds more complexity & readability to calculations used to determine vector widths and array sizes
- Arguments must be constants at elaboration time (e.g. parameters)
- Added in Verilog-2001
  - Previously only constant expressions based on arithmetic operators supported for object definitions

# Generate Constructs

- Used to create structural blocks
  - Each module generated creates a level of hierarchy
    - Similar to performing separate module/primitive instantiations
    - Reduces amount of code
  - Resolved at elaboration (compile) time
    - Must resolve to a constant number of blocks
  - Use **generate-endgenerate** (generate regions) to explicitly define generate region<sup>1</sup>
    - Cannot nest generate regions

<sup>1</sup> Generate regions are considered optional by the Verilog specification, but are required by the Quartus II software

# Generate Constructs (cont.)

- Generate blocks can contain
  - Module declarations
  - Module/primitive instantiations
  - Parameter overrides
  - Assign statements
  - Procedural blocks
- Generate blocks cannot contain
  - Port declarations
  - Parameter declarations

# Generate Constructs Types

## ■ if-generate

- Conditionally selects whether structure is made or not

## ■ case-generate

- Conditionally selects which structure from multiple choices is made

## ■ Loop-generate

- Creates zero or a set number of duplicates of a structure
- No need to individual instantiate each duplicate

## ■ Can be nested for further complexity

# if-generate Construct

## ■ Syntax

```
generate  
  if <expression>  
    // generated structure  
  else  
    // alternate generate structure  
endgenerate
```

## ■ Condition controls whether structure is created

- Same syntax as procedural block **if-else**
- Each structure may contain only one item
  - Surround multiple statements with begin/end



# if-generate Example 1

```
module counter
  #(parameter WIDTH = 8, RISE_OR_FALL = 1)
  (
    input clk, clr, sload, cnt_en,
    input [WIDTH-1:0] data,
    output reg [WIDTH-1:0] q
  );

  wire clk_buf;

  generate
    // Rising or falling clock generation logic
    if (RISE_OR_FALL)
      assign clk_buf = clk;
    else
      assign clk_buf = ~clk;
  endgenerate

  always @ (posedge clk_buf or negedge clr)
  begin
    if (!clr)
      q <= 0;
    else if (sload)
      q <= data;
    else if (cnt_en)
      q <= q + 1'b1;
  end
endmodule
```

rising or falling  
edge clock

- Simple code slice to implement both rising & falling edge counter
  - Generate block with ASSIGN statements
- Different than using if-else
  - No mux (or gated) clock created

# if-generate Example 2

```
generate
  if (PIPELINE = "YES")
    begin: pipelined_mult
      mult_clk #(.AWIDTH(D_WIDTHHA), .BWIDTH(D_WIDTHHB))
      u1 (.dataa(dataa), .datab(datab), .aclr(aclr),
        .clken(clken), .clock(clock), .result(result));
    end

  if (PIPELINE = "NO")
    begin: combinational_mult
      comb_mult #(.AWIDTH(D_WIDTHHA), .BWIDTH(D_WIDTHHB))
      u1 (.dataa(dataa), .datab(datab), result(result));
    end
endgenerate
```

- This code uses a text string (PIPELINE) to call a pipelined or non-pipelined implementation of a multiplier block
  - Generate block with module instantiations
- One or the other (or neither) gets instantiated in design
- Begin/end unnecessary since one statement in each, but needed to name generate block
  - Block name not required

# case-generate Construct

## ■ Syntax

```
generate  
  case <expression>  
    <condition1> : // generated structure  
    <condition2> : // generated structure  
    <conditionN> : // generated structure  
    default : // generated structures  
endgenerate
```

## ■ Condition controls which structure is created

- Same syntax as procedural block **case**
- Each structure may contain only one item
  - Surround multiple statements with begin/end

# case-generate example

```
module data_conversion
  #(parameter DATA_PATH = 8)
  (
    input clk, reset, clk_en,
    input [DATA_PATH-1:0] data,
    output reg [DATA_PATH-1:0] result
  );

  generate // Data conversion of bytes received serially
    case (DATA_PATH)
      8 : byte_convert u1(.datain(data), .dataout(result),
        .clk(clk), .clken(clken), .clr(reset));
      16 : hword_convert u1(.datain(data), .dataout(result),
        .clk(clk), .clken(clken), .clr(reset));
      32 : word_convert u1(.datain(data), .dataout(result),
        .clk(clk), .clken(clken), .clr(reset));
    endcase
  endgenerate
endmodule
```

- Case statement performs test to see which of the byte conversion blocks get instantiated in the design
- Notice all 3 possible instances named “u1”
  - Legal as only one will exist in compiled design

# Loop-generate (for-generate)

## ■ Syntax

```
genvar i; // Required
generate
  for (i=<init_val>; <exp using i>; <inc using i>)
  begin : <generate_block_name> // Required
    // generate structure
  end
endgenerate
```

- Sets the number of structures created
  - Similar to procedural block for loop
  - Can only use concurrent statements
- Generate block must be named for loop-generate
- Requires **genvar** declaration
  - Index used as integer count during loops
    - Does not exist once code is elaborated
  - One **genvar** cannot be shared by multiple loop constructs
    - Use multiple **genvar** variables for multiple loops

# For Generate Example

```
module ram16x8
  #(parameter DWIDTH = 8, AWIDTH = 4)
  (
    input tclk, twe,
    input [DWIDTH-1:0] tdata,
    input [AWIDTH-1:0] taddress,
    output [DWIDTH-1:0] tq
  );

  genvar j;

  generate
    for (j=0; j<DWIDTH; j=j+1)
      begin : memory_gen // Generate block name
        → ram #(.WIDTH_AD(AWIDTH))
          u1 (.clk(tclk), .we(twe), .data(tdata[j],
            .address(taddress), .q(tq[j]));
      end
    endgenerate

endmodule
```


```
module ram ←
  #(parameter WIDTH_AD = 2)
  (
    input clk, we, data,
    input [WIDTH_AD-1:0] address,
    output reg q
  );
```

Signal Bit RAM

8 single-bit RAMs  
generated

# 8 - 16x1 RAM Functions

Memory Block Names

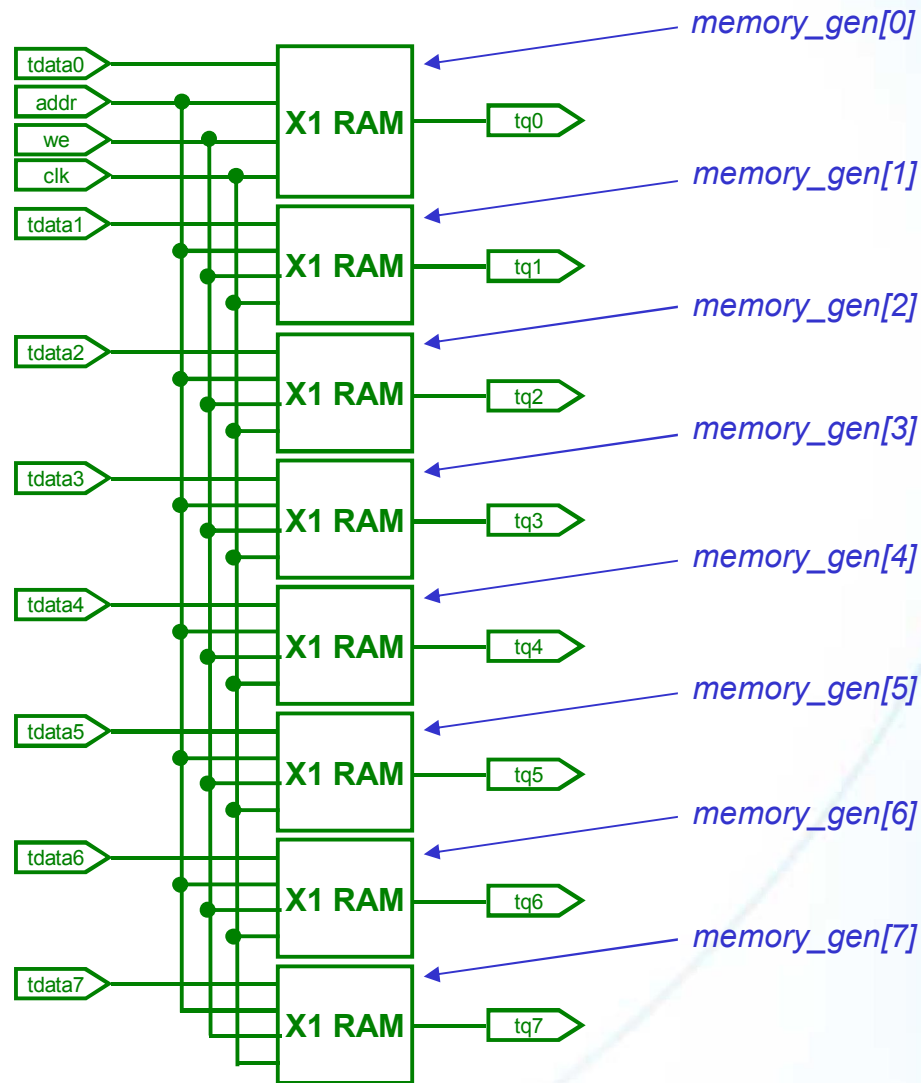




# Nested Generate Statements

```
module dffn (  
    input clk, d,  
    output reg q  
);  
    always @ (posedge clk)  
        q <= d;  
endmodule
```

```
module shift_reg  
    #(parameter LENGTH = 16)  
    (  
        input in, clk,  
        output out  
    );  
  
    wire [LENGTH-1:1] sig;  
    genvar n;  
  
    generate  
        for (n=0; n<LENGTH; n=n+1)  
            begin: shift_reg_gen  
                case (n)  
                    0 : dffn u1 (.q(sig[n+1]), .clk(clk), .d(in));  
                    LENGTH-1 : dffn u1 (.q(out), .clk(clk), .d(sig[n]));  
                    default : dffn u1 (.q(sig[n+1]), .clk(clk), .d(sig[n]));  
                endcase  
            end  
        endgenerate  
    endmodule
```

© 2009 Altera Corporation—Confidential

Code generates  
a shift register

 

generates first register

generates last register

generates intermediate  
register(s)


# Nested Generate Statements (Alt.)

```
module shift_reg
  #(parameter LENGTH = 16)
  (
    input in, clk,
    output out
  );

  reg [LENGTH-1:1] sig;
  genvar n;

  generate
    for (n=0; n<LENGTH; n=n+1)
      begin: shift_reg_gen
        case (n)
          0 : always @ (posedge clk)
            sig[n+1] <= in;
          LENGTH-1 : always @ (posedge clk)
            out <= sig[n];
          default : always @ (posedge clk)
            sig[n+1] <= sig[n];
        endcase
      end
    endgenerate
endmodule
```
 
## Alternate code generates a shift register



- This example illustrates how procedural (always) blocks can also be used in generate statements
- Same as writing individual procedural blocks
  - Code expanded at elaboration

# Summary

- More advanced Verilog language concepts than versus introductory class
- Efficient coding styles for good synthesis
- Testbench creation for simulation
- Building re-usable code